

**EXPERIMENT 11: LINEAR OP-AMP CIRCUITS**

(revised 11/20/07)

In this experiment we will examine the properties of operational amplifier circuits with various feedback networks. Circuits which perform four basic linear mathematical operations - addition, subtraction, integration, and differentiation - will be studied.

We will use a model  $\mu A741$ , operational amplifier. This is a general purpose, integrated-circuit op-amp with detailed specifications listed in the appendix to this experiment. The op-amp requires a  $\pm 15$  V power source. We will use a small power supply that provides these voltages plus a zero to  $\pm 5$  V variable DC output. The op-amp will supply a maximum output current of about 25 mA and has typical offset currents of about 20 nA. This implies that resistors in the range 1 k $\Omega$  to 100 k $\Omega$  should be used.


Use a scope for all measurements.

1. (a) Construct the operational feedback amplifier shown below with  $R_1 = 1$  k $\Omega$  and  $R_2 = 20$  k $\Omega$  with  $v_{in}$  grounded, adjust the pot on the circuit board for zero output voltage. Using sine waves from the function generator for  $v_{in}$  (with the amplitude set for 0.5 Volts peak-to-peak), measure and tabulate the amplitude and phase of  $v_{out}$  for  $100$  Hz  $\leq f \leq 100$  kHz (take about 3 points/decade).
- (b) For a feedback amplifier the gain is given by:

$$A(\omega) = \frac{v_{out}}{v_{in}} = - \frac{R_2 A_0(\omega)}{R_1 A_0(\omega) + (R_1 + R_2)}$$

where  $A_0(\omega)$  is the open loop gain and  $A(\omega)$  is the closed loop gain. Use this formula and your measured values of  $A(\omega)$  to find  $A_0(\omega)$  at 20 kHz and 100 kHz. Assuming that  $A_0(\omega)$  varies with frequency according to:
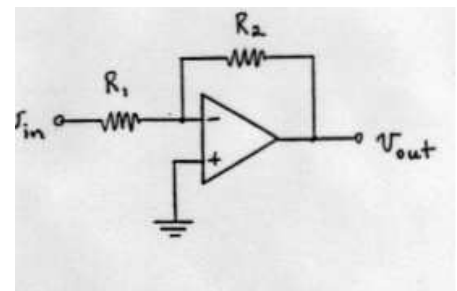
$$A_0(\omega) = \frac{A_0}{(1 + j \frac{\omega}{\omega_c})}$$




where  $\omega_c = 10\pi$  radians/s, find the DC mid-band open-loop gain,  $A_0$ . Compare your result to the typical value given in the appendix.

2. Change  $R_2$  to 10 k $\Omega$  and set  $f = 1$  kHz. Increase the amplitude of  $v_{in}$  until  $v_{out}$  exhibits saturation at both positive and negative voltages. Sketch and determine the saturation voltages.


## OPERATIONAL AMPLIFIERS

3. (a) The slew rate of the amplifier is defined as the maximum rate of change of the output voltage. Switch the input to square waves and set  $f = 10 \text{ kHz}$ . Adjust the amplitude to obtain a peak-to-peak output voltage of 10 Volts. Measure the slew rate by observing  $dv_{\text{out}}/dt$  and compare your result to the typical value listed in the appendix.
- (b) Suppose you want to use the amplifier to produce a sine wave output with an amplitude of 10 Volts peak-to-peak. What is the maximum frequency you can use before the output wave begins to be distorted by the finite slew rate of the amplifier? Switch the input to sine waves and observe what happens when you exceed that frequency. Sketch the input and output waveforms.
4. Set up the summing amp circuit shown below with  $R_i = R_f = 10 \text{ k}\Omega$ . Use the Lambda DC power supply for  $V_1$ , and the  $\pm 5 \text{ V}$  supply for  $V_2$ . Measure  $V_{\text{out}}$  for three or four different values of  $V_1$  and  $V_2$  (using both positive and negative values of  $V_2$ ) and verify that  $V_{\text{out}} = -R_f(V_1 + V_2)/R_i$ .
5. Set up the circuit shown below for subtracting two voltages. As in the previous step, use  $R_i = R_f = 10 \text{ k}\Omega$ . Measure  $V_{\text{out}}$  for three or four different values of  $V_1$  and  $V_2$ , and verify that  $V_{\text{out}} = R_f(V_2 - V_1)/R_i$ .

**adder or summing amp**

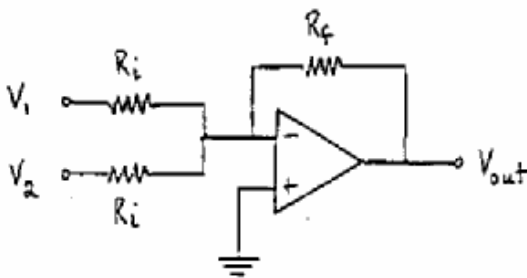

**subtractor**

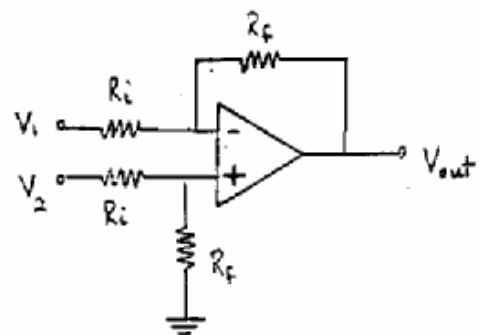


OPERATIONAL AMPLIFIERS

6. (a) Set up the differentiator circuit shown below with  $C = 100 \text{ nF}$  and  $R = 2 \text{ k}\Omega$ . For the input use a 2 Volt peak-to-peak,  $f = 1 \text{ kHz}$  triangle wave. Sketch the input and output waves and measure the magnitude of  $v_{out}$ . Compare your measured value with the expected result,  $v_{out} = -RC \times dv_{in}/dt$ . Also, measure and tabulate the values of  $v_{out}$  (no sketches required) for  $f = 2 \text{ kHz}$  with  $C = 100 \text{ nF}$ , and for  $f = 2 \text{ kHz}$  with  $C = 50 \text{ nF}$ .
- (b) Switch the input waveform to square wave and sketch  $v_{in}$  and  $v_{out}$ . Explain why  $v_{out}$  looks the way it does.
7. (a) Set up the integrator circuit shown below, with  $C = 100 \text{ nF}$ ,  $R_F = 200 \text{ k}\Omega$ , and  $R = 10 \text{ k}\Omega$ . Use a 2 Volt peak-to-peak,  $f = 1 \text{ kHz}$  square wave for  $v_{in}$ . Sketch the input and output wave forms and determine the magnitude of  $v_{out}$ . Compare your measurement with the expected result  $v_{out} = -(1/RC) \times \int v_{in} dt$ .
- (b) Observe what happens to the output voltage as you make  $R_F$  larger and smaller. What happens when  $R_F$  is removed? Explain why we need to have a feedback resistor in any integrating circuit.
- (c) Switch the input waveform to triangle wave and sketch the resulting input and output waveforms. In this case  $v_{out}$  looks quite similar to a sine wave. See if you can understand this result by writing down the Fourier expansion of a triangle wave and integrating this expression.

**differentiator**

**integrator**

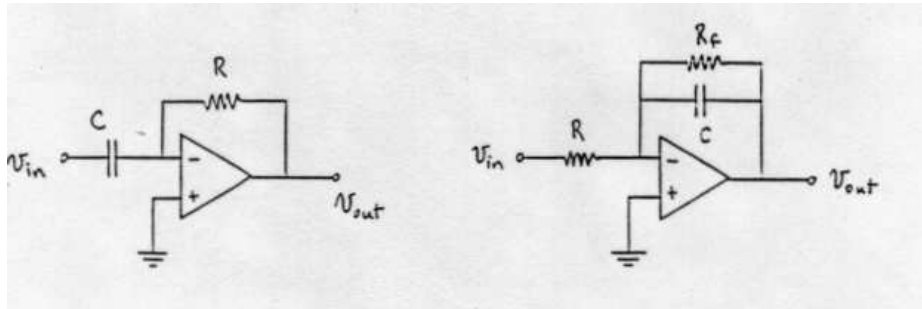

OPERATIONAL AMPLIFIERS

**APPENDIX** — Specifications for the  $\mu$ A741 op-amp

$V_{CC} = \pm 15V$ ,  $T = 25^\circ C$

<b>PARAMETER and CONDITIONS</b>	<b>MIN</b>	<b>TYP</b>	<b>MAX</b>	<b>UNITS</b>
Input Offset Voltage $R_s = 10\text{ k}\Omega$		1.0	5.0	mV
Input Offset Current		20	200	nA
Input Bias Current		80	500	nA
Input Resistance	0.3	2.0		M $\Omega$
Input Capacitance		1.4		pF
Offset Voltage Adjustment Range		$\pm 15$		mV
Output Resistance		75		$\Omega$
Output Short Circuit Current		25		mA
Large Signal Gain $R_L \geq 2\text{ k}\Omega$ , $V_{out} \leq \pm 10\text{ V}$	$5 \times 10^4$	$2 \times 10^5$		
Output Swing (Vsat) $R_L = 2\text{ k}\Omega$	$\pm 10$	$\pm 13$		V
$R_L = 10\text{ k}\Omega$	$\pm 12$	$\pm 14$		V
Slew Rate $R_L = 2\text{ k}\Omega$		0.5		V/ $\mu$ s
Transient Response $V_{in} = 20\text{ mV}$ , $R_L = 2\text{ k}\Omega$ , $C_L \leq 20\text{ pF}$ , unity gain				
Risetime		0.3		$\mu$ s
Overshoot		5		%
Common Mode Rejection Ratio	70	90		dB
Power Supply Rejection Ratio		30	150	$\mu$ V/V
Supply Current		1.7	2.8	mA
Power Consumption		50	85	mW