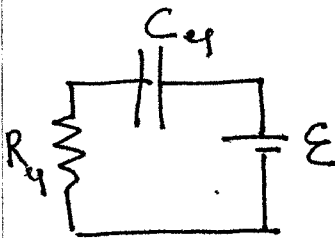


Review Session

Issues discussed:

① RC circuits. You should know →


single loop RC circuit
(perhaps w/ equiv. $R_{eq} + C_{eq} \rightarrow$
reducing series + parallel combinations)



$$\tau = R_{eq} C_{eq}$$

Charging → Initial charge 0
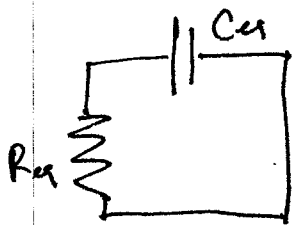
$$Q(t) = \epsilon C_{eq} (1 - e^{-t/\tau})$$



Discharging → initial charge Q_0


$$Q(t) = Q_0 e^{-t/\tau}$$

$$I(t) = \frac{dQ(t)}{dt}$$

② Hall Effect → basic physics.

Know that E field induced

s.t. essentially $qE_{hall} = qv_d B$

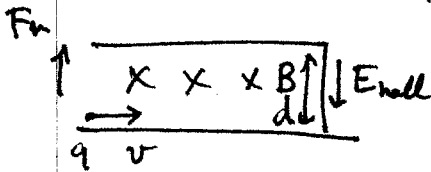

$$E_{hall} = \frac{V_{Hall}}{d} \quad v_d = \frac{I}{nqA}$$


$$A = \text{Area} = dt$$

↓ thickness →


$$V_H = \frac{IB}{nqt}$$

③ Kirchhoff Rules.

Recognize series

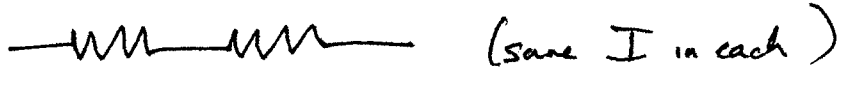

Recognize parallel

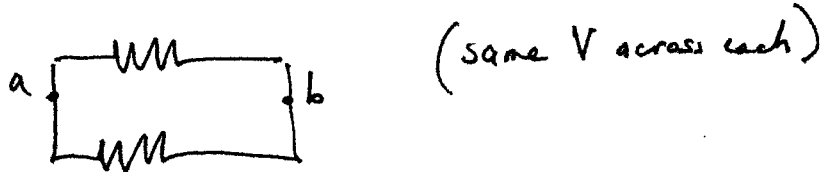

often useful to reduce more complicated circuits. (Can still use Kirchhoff even if you don't reduce, of course)

General

- Assign currents clearly. ~~Label~~ Label figure!!
 - Apply junction conditions
 - Apply loop rule for each indep circuit.
- can combine these steps.

Examples.

26.82



Asked for $\rightarrow R_{eq}$

$R_1 + R_2$ in parallel but others not so easily reducible.

Just do it using Kirchhoff \rightarrow

Assign currents



loops \rightarrow ① $V - (I - I_1 - I_2)R_3 = 0$
right loop

② $V - I_1 R_1 - (I + I_2)R_4 = 0$
(outer edge)

③ $-I_2 R_2 - (I_1 + I_2)R_4 + (I - I_1 - I_2)R_3 = 0$
triangular loop


Solve.

Getting this far is


75% - 80% credit.

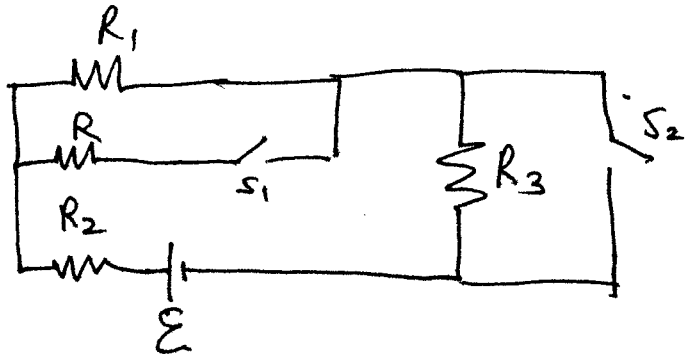26.80

Given \rightarrow current through R_1 see depends on whether both switches or both open. Given: $R_1, R_2, R_3, \mathcal{E}$.
asked for $\rightarrow R$.




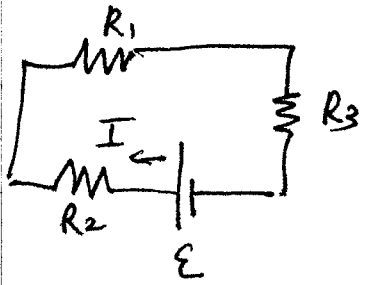Both open \rightarrow equiv circuit (open switch = no current through that branch)



$$\mathcal{E} - I(R_1 + R_2 + R_3) = 0 \quad (*)$$

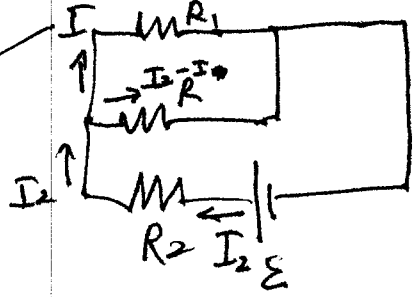Both closed \rightarrow short out R_3 , open up R branch:



$$\begin{aligned} \mathcal{E} - I_2 R_2 - I R_1 &= 0 \\ I_1 R_1 - (I_2 - I) R &= 0 \end{aligned}$$

eliminate I_2 , solve \rightarrow for R .

Last

Practice midterm Problem #4.

Very Important!! Do it!!

(See MT exam soln).

to the end. Good luck!!!