

Prelab – Experiment 9

Single Transistor Amplifiers

Read the Experiment 9 instructions thoroughly and then answer the following questions:

1 Question 1

Assume that Fig 8.6(a) in Sprott contains a silicon transistor with $V_{BE} = 0.6\text{ V}$ and $\beta = 200$. The other circuit components are $R_1 = 20\text{ k}\Omega$, $R_2 = 1.6\text{ k}\Omega$, $R_C = 2\text{ k}\Omega$, $R_E = 200\text{ }\Omega$, and $V_{CC} = 21.6\text{ V}$.

Calculate the voltage gain, A , input resistance, R_{in} , and transresistance, $r_{tr} \approx r_d$ (Refer to Eqs 8.2 and 8.3 in Sprott, but neglect r_{ohmic}). Also calculate the value of V_C at cut off ($I_C = 0$) and at saturation ($V_{CE} = 0.2\text{ V}$).