

Physics 321 — Lab 12 — Prelab Worksheet

Draw the circuit for a three-bit shift register using three J-K flip flops. Briefly describe its operation.