

# Prelab – Experiment 10

## Operational Amplifier Circuits

### 1 Question 1

Derive the closed-loop gain for the operational feedback (inverting) amplifier

$$A(\omega) = \frac{V_{\text{out}}}{V_{\text{in}}} \approx -\frac{A_0(\omega)R_2}{A_0(\omega)R_1 + R_2} \quad (1)$$

This is Eq. 9.8 in Sprott but generalized to allow the open-loop gain to be frequency dependent (see Fig. 9.15 for a typical example).

Hint: Fill in the missing algebraic steps in Sprott's derivation using the equivalent circuit shown in Fig. 9.5(b), including the approximation  $A_0 + 1 \approx A_0$ .

### 2 Question 2

Take the open-loop gain to be

$$A_0(\omega) = \frac{A_{0,\text{dc}}}{1 + j(\omega/\omega_0)} \quad (2)$$

and show that for  $\omega \gg \omega_0$

$$A(\omega) = \frac{R_2/R_1 e^{j\phi}}{\sqrt{1 + (\omega/\omega_c)^2}}, \quad \omega_c = \frac{R_1}{R_2} A_{0,\text{dc}} \omega_0, \quad \phi = \pi - \tan^{-1} \left( \frac{\omega}{\omega_c} \right) \quad (3)$$

This resembles the response of a low-pass filter but with low-frequency gain,  $A = R_2/R_1$ .