

Ph 623 - 14 April

Labs - Can't get PLL working reasonably
Is simulation of D/A - A/D lab worthwhile
Alternative is 3 FPGA labs

Try to get simulation lab done by end of week.
Send me questions

H+H P.I.D. Controller for temperature 15.6.2

S.A.R. in A/D : 13.7


Dual Slope (integrating) A/D : 13.84

Σ - Δ ADC 13.9 ffff ← Good explanation, but
requires considerable
time investment - won't
get much out of skimming.

Mathematician's Approach:

— reduce it to a problem you've solved before


Something you'll need for sim. lab

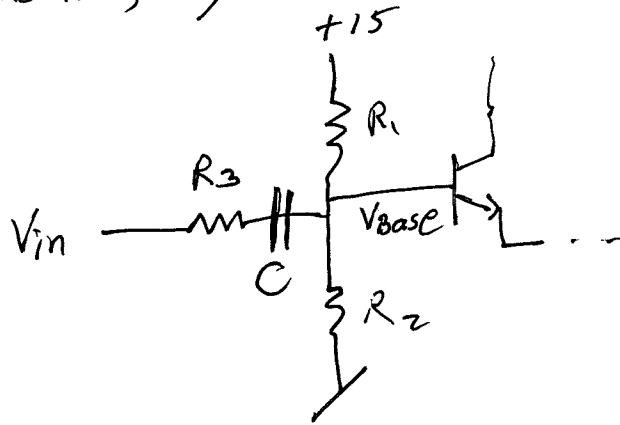


What is $\frac{V_{base}}{V_{in}}(\omega)$

You know: $\frac{C}{R} = \frac{R}{R + \frac{1}{i\omega C}} = \frac{i\omega RC}{1 + i\omega RC}$

~~Series~~
A.C. problem, so
+15 = GND

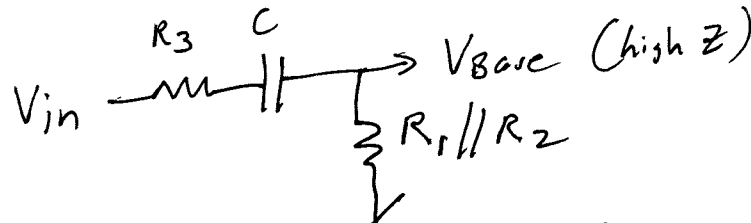

Hi-F limit:

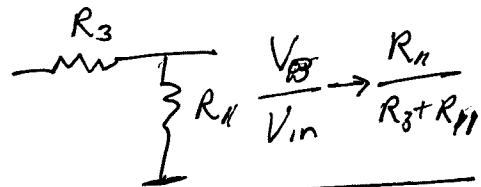

Capacitor has to charge thru both resistors in series, so expect $\tau = (R_3 + R_{11})C$.

\therefore Expect $\frac{V_{Base}}{V_{in}} = \frac{R_{11}}{R_3 + R_{11}} \cdot \frac{i\omega(R_3 + R_{11})C}{1 + i\omega(R_3 + R_{11})C}$

So lower corner should be at $\omega = \frac{1}{(R_3 + R_{11})C}$


Voltage Divider Eq:

$$\frac{V_B}{V_{in}} = \frac{R_{11}}{R_{11} + R_3 + \frac{1}{i\omega C}} = \frac{i\omega C R_{11}}{1 + i\omega C (R_{11} + R_3)}$$

$$= \frac{i\omega C R_{11} \frac{(R_{11} + R_3)}{R_{11}}}{1 + i\omega C (R_{11} + R_3)} \cdot \frac{R_{11}}{R_{11} + R_3}$$

Miller Effect: 2.4.5

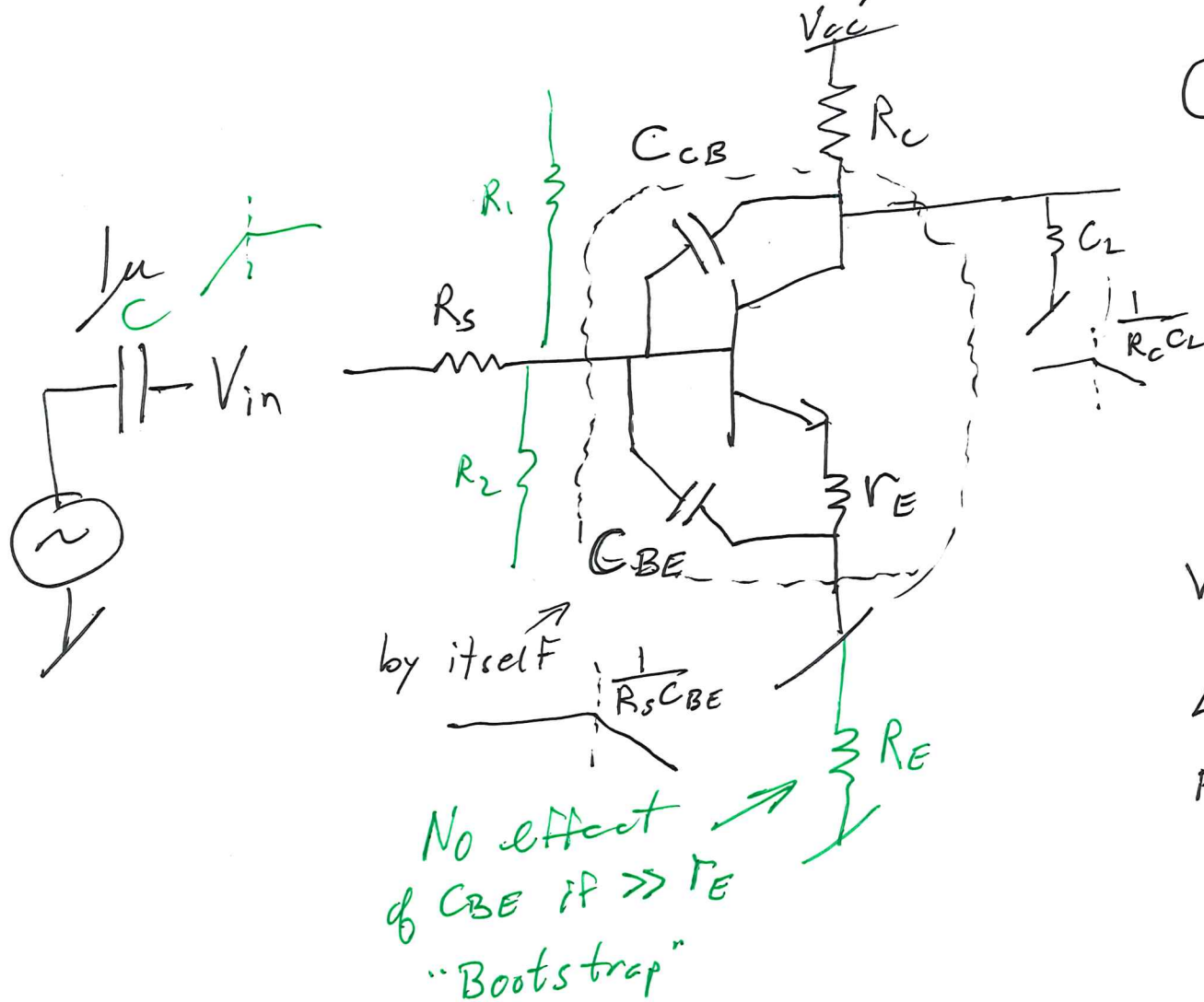Will investigate in analog simulation of the differential amplifier you built



C_{CB} is bigger
problem: $A = \frac{-R_C}{R_E + R_E}$
 $\gg 1$

$V_B \uparrow$ by ΔV
 $V_C \downarrow$ by $A \Delta V$
 $V_{CCB} \uparrow (A+1) \Delta V$

$\Delta Q_{CCB} = (A+1) C_{CB} \Delta V$
From Base looks like $(A+1) \times$ bigger


$$= \frac{1}{R_s (A+1) C_{CB}}$$

You will investigate this behavior of ~~the~~ differential amplifier in sim lab: run with $R_s = 0$ and $R_s = 1\text{K}$. High-frequency behavior quite different. See if you can predict \rightarrow upper corner F for $R_s = 1\text{K}$ (Model for 2N3904 has $C_{cb} = 3.6\text{pF}$ - you can edit!)


This is big problem for high-freq amplifiers.

Fixes:

"Cascode"

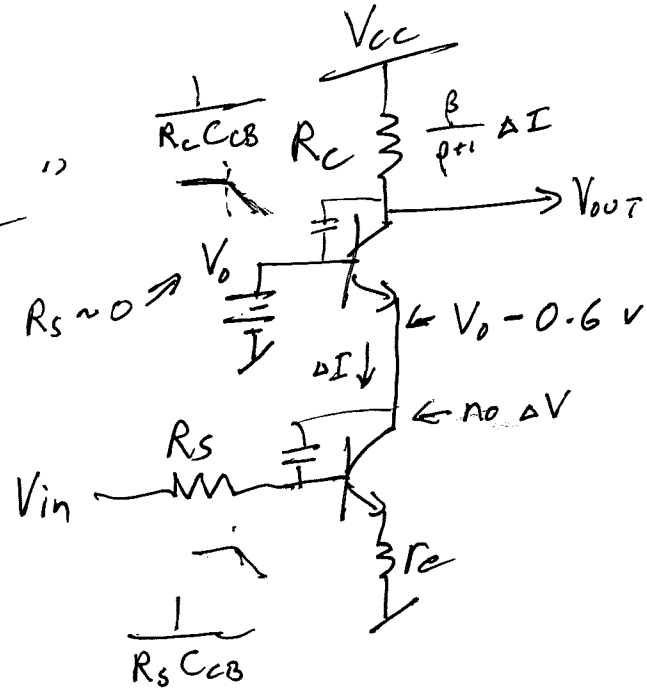

#2 Diff amp

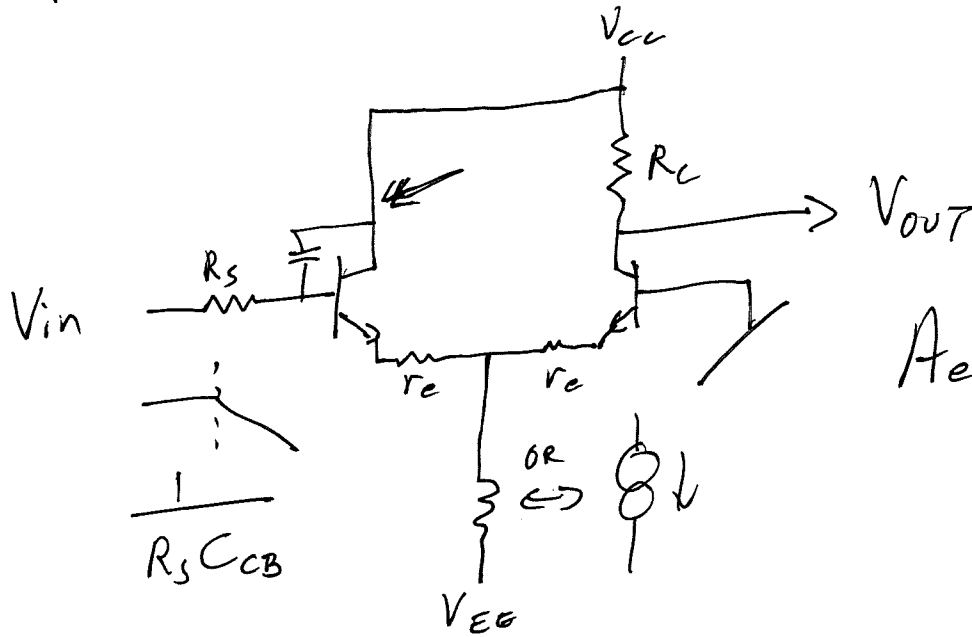




$$V_{Diff} = V_{in} - 0$$

$$V_{cm} = \frac{V_{in} + 0}{2}$$



$$A_{eff} = A_{dm} - \frac{1}{2} |A_{cm}|$$

$$A_{cm} \ll A_{dm}$$


÷ 6

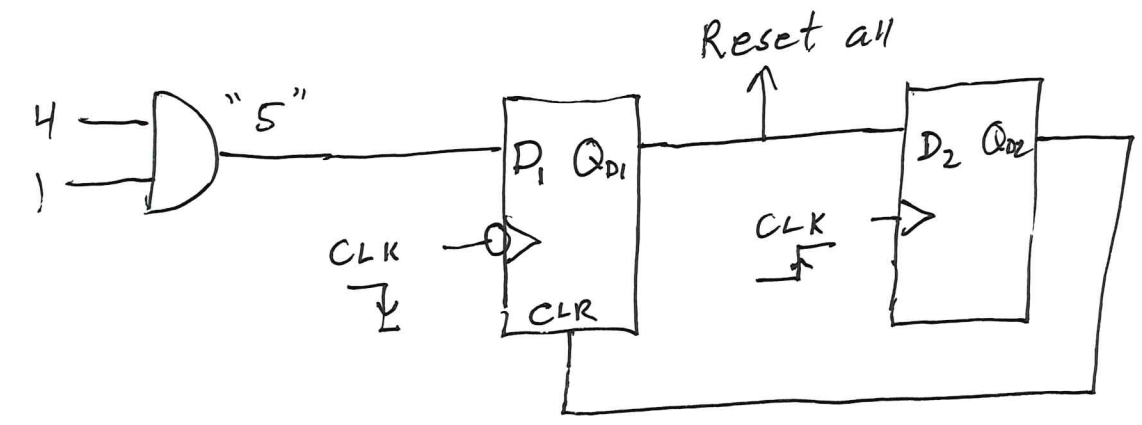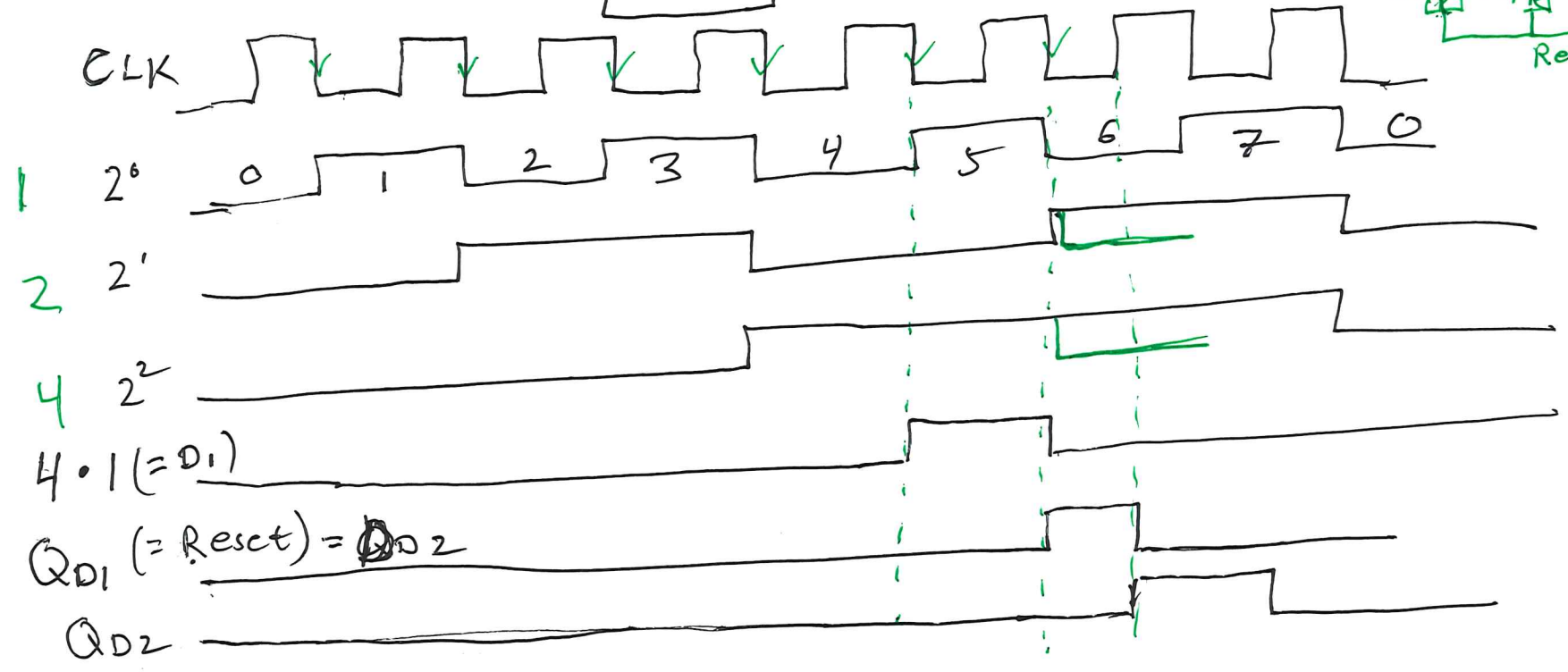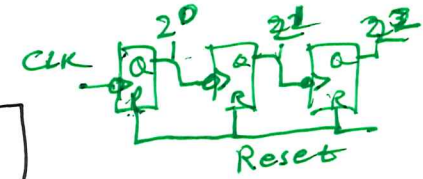


"Switch Bounce"

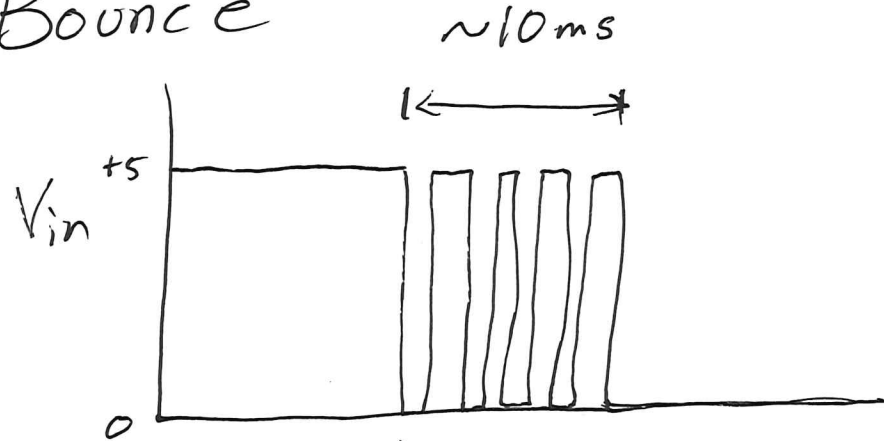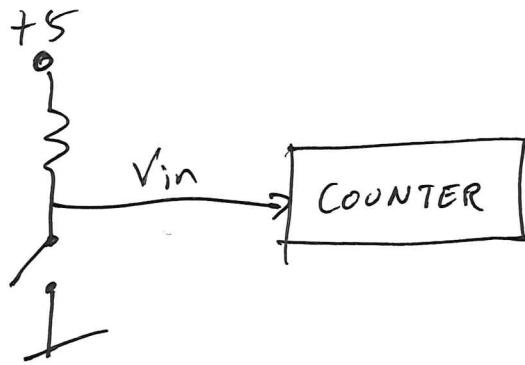


"De-Bounce"

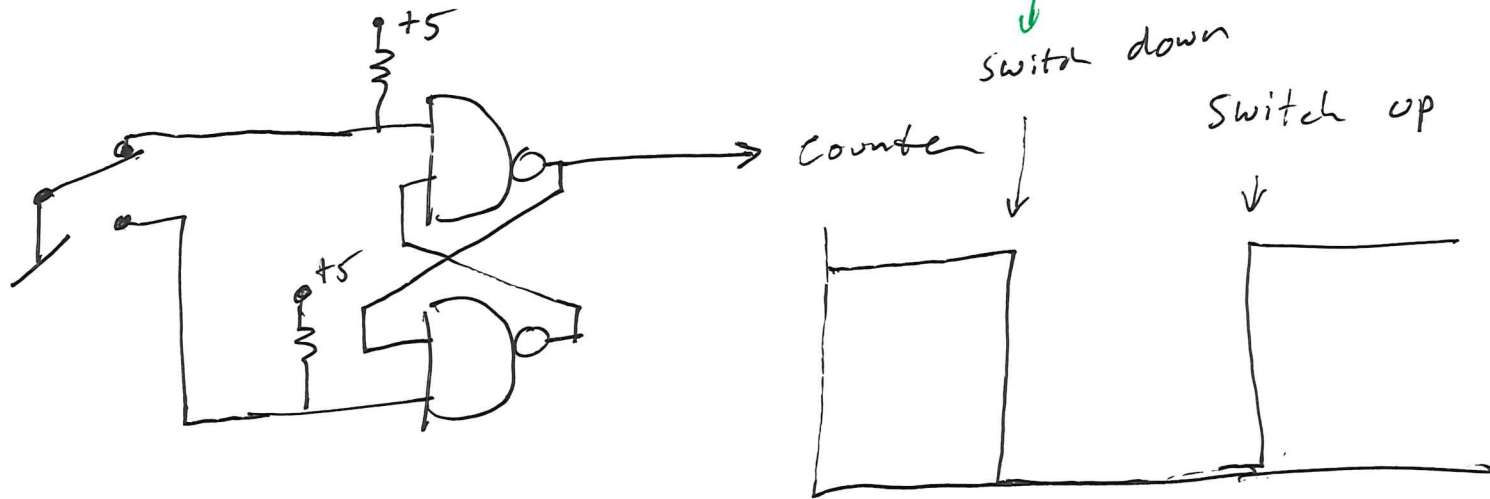


"Glitches"

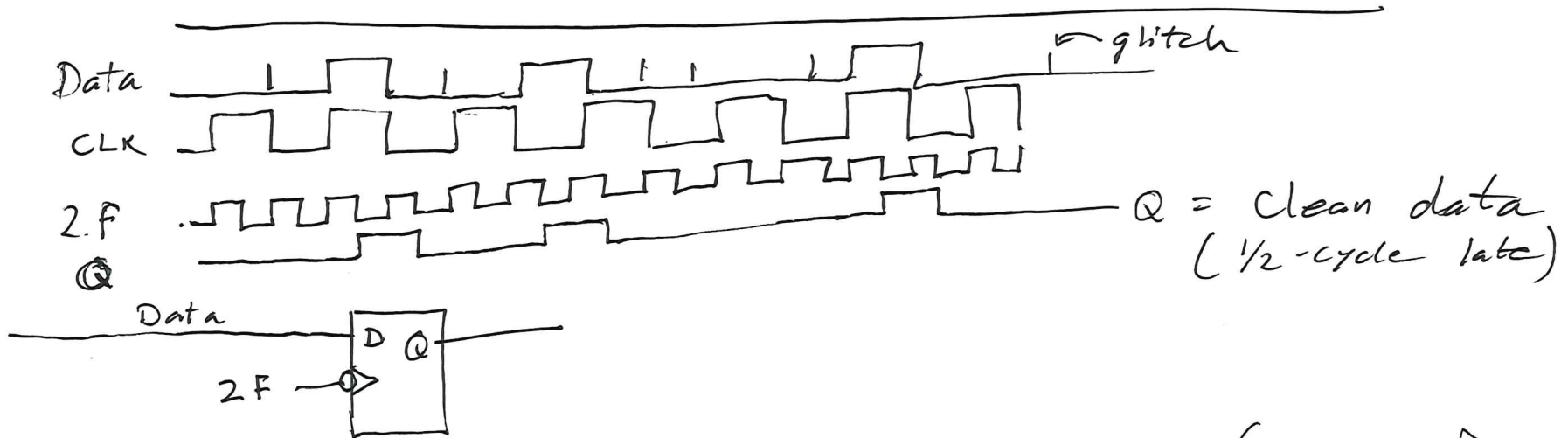

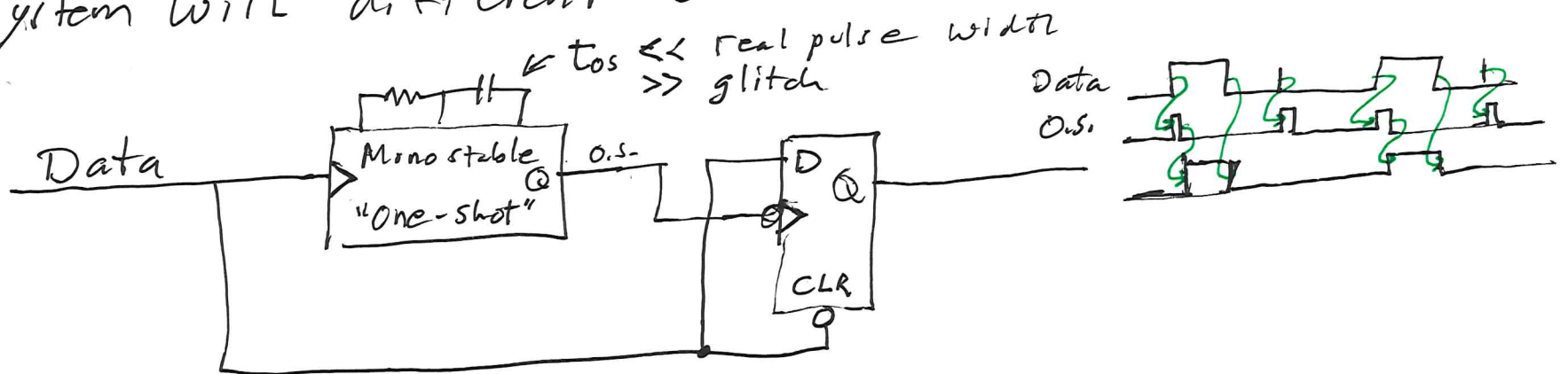IF data not synchronous (comes from system with different clock):



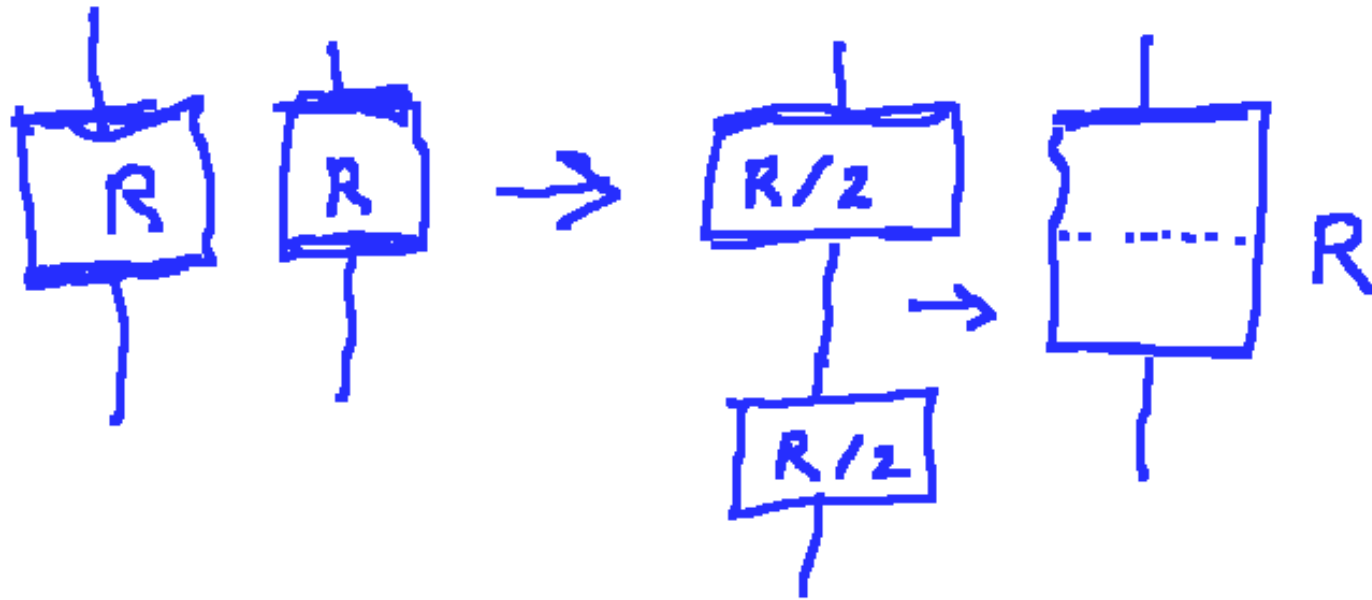


"Sheet Resistance" = "ohms/square"
(independent of size of square)

$$C_{gate} \sim A/d \sim L^2$$

$$\tau \sim RC \Rightarrow \text{speed} \sim 1/L^2$$

(since R is indep of L)

$$\text{Devices/Area} \sim 1/L^2$$

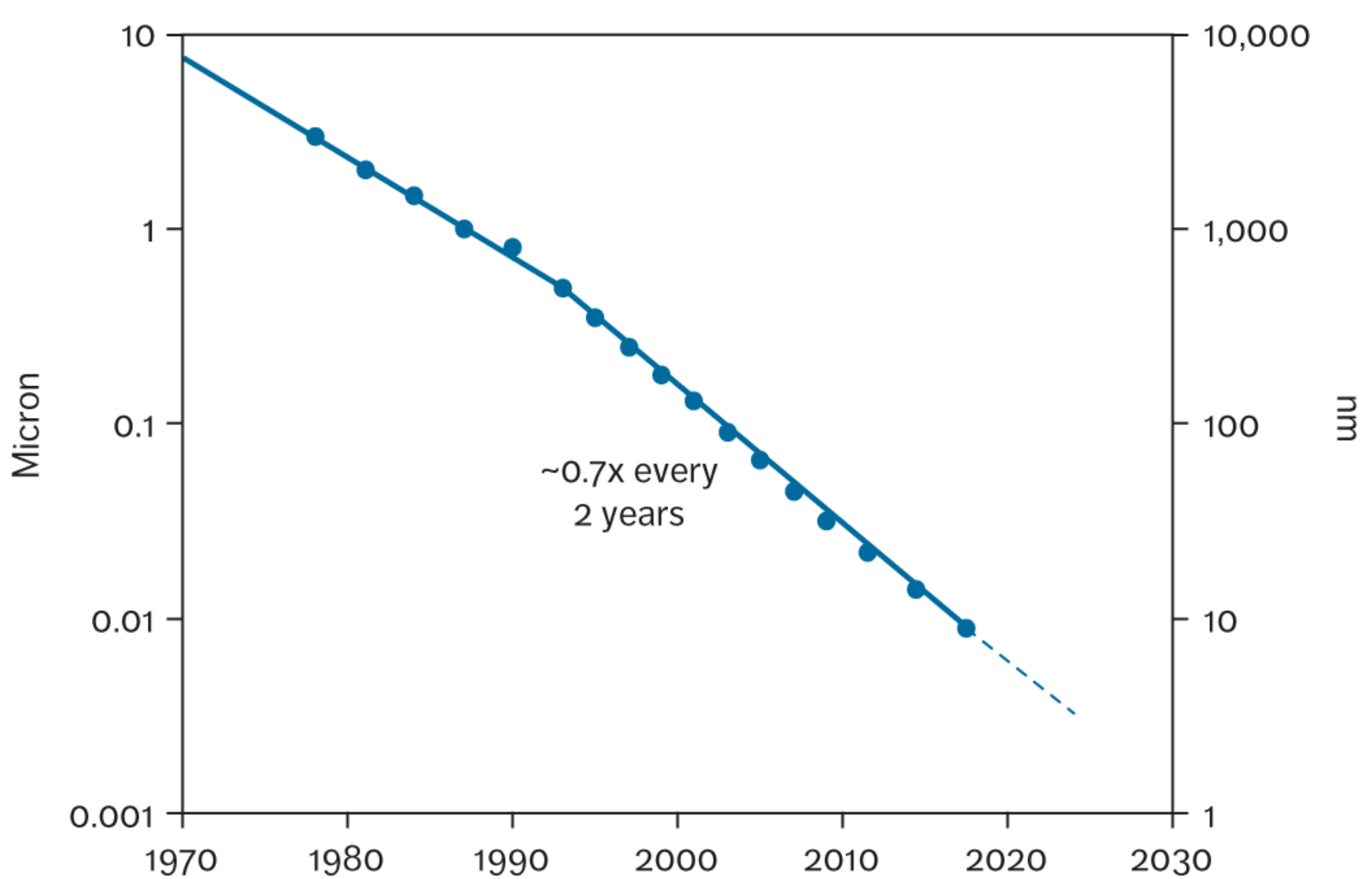

Problem:

Energy of transition = $\frac{1}{2} CV^2$

Power $\sim CV^2 f_{\max} \sim L^2 V^2 (1/L^2) \sim V^2$

But: Device density $\sim 1/L^2$

\Rightarrow power density $\sim V^2/L^2$

So need to reduce V :

$5\text{ V} \rightarrow 3.3\text{ V} \rightarrow 2.2\text{ V} \rightarrow 1.8\text{ V} \rightarrow 1.2\text{ V} \rightarrow 0.8\text{ V}$

Requires thinner oxide

