

Ph 623 - 28 April 2020 ("Day 36")

---

- No HW
- FPGA II+III (or Combo)  
due at Final exam
- Final Exam: 7:45 AM CDT  
Monday May 4<sup>th</sup>
  - Closed book
  - calculator and  
one 3x5 card  
(both sides)
  - 2h +  $\frac{1}{2}$ h

Today

- Communication

Balanced Modulator

AM

FM

SSB

Heterodyne

Homodyne

Bi-Phase

NRZ

Class A, B, AB, C, D  
amplifiers

PWM

Error Correction

Modulation Factor


# Modulation

AM




Carrier (1 MHz)

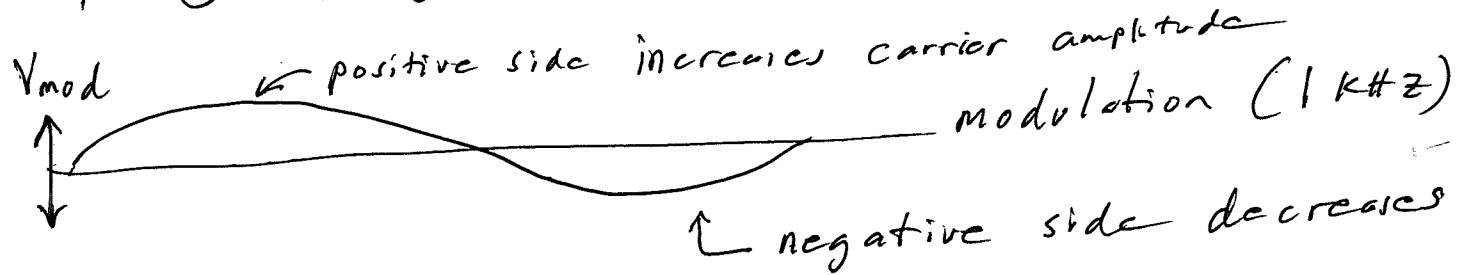Actually usually  
a mixture of  
frequencies and  
amplitudes  
(voice, music)



positive

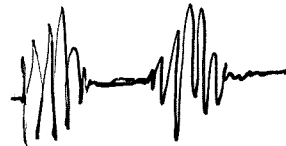{ say, 50 Hz - 10 kHz  
0 -  $A_{max}$  peak



distortion - many frequency  
components not in  
original:  
"over-modulation"

∴ need  $(A_{max} + V_{max}) \times \text{carrier}$

Suppose  $A_{max} = 1 \text{ Volt}$





Say  $F_{max} = 10 \text{ kHz}$

and we have  $V_{mod} = 1 \text{ V pk @ } F_{max}$

What does transmitted signal look like?

?

X

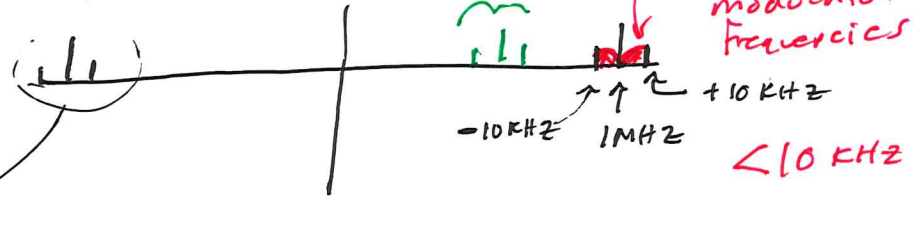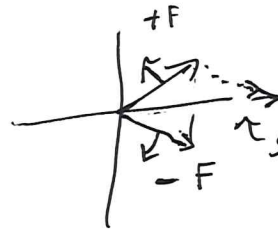
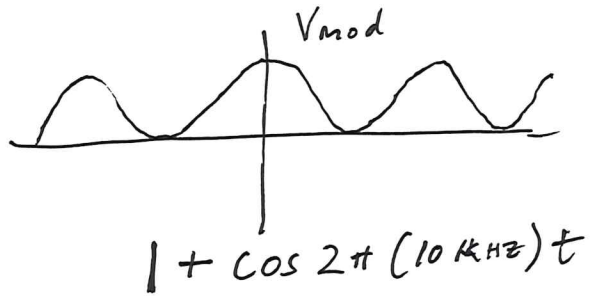
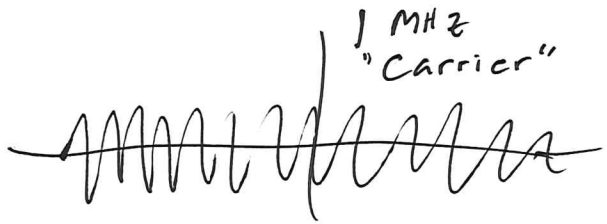


redundant info.




bandwidth is double BW of information


Advantages: simple efficient\*

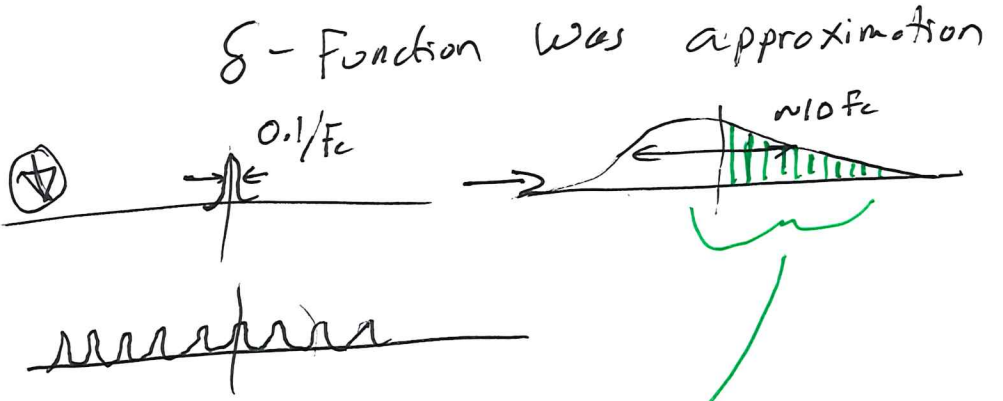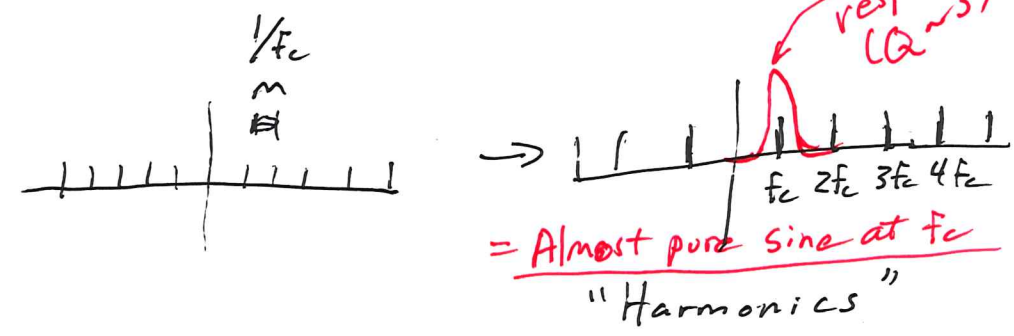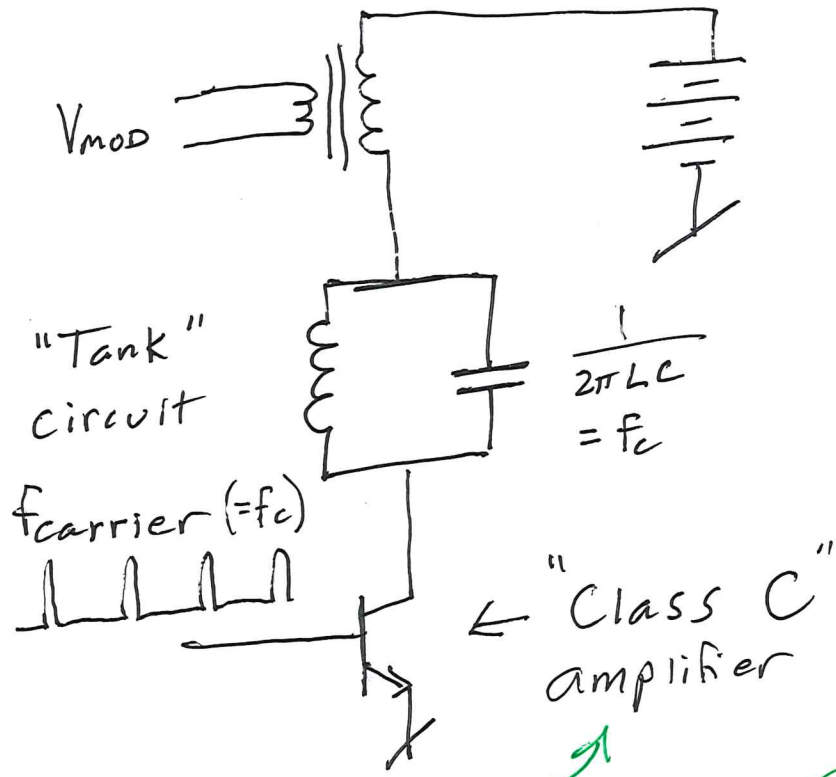

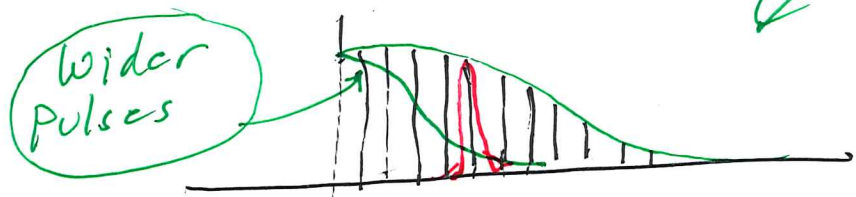
Very efficient use of output transistor - switch on or off - no power lost in switch - no heat to get rid of.




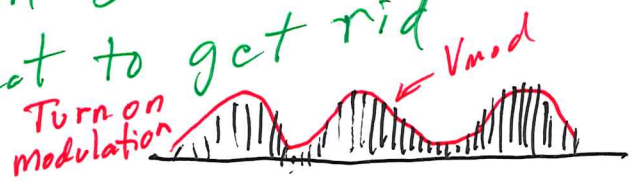
Frequency Multiplier  
- tune tank to  $5 f_c$   
(need higher Q to keep pure)



Demodulation also simple:

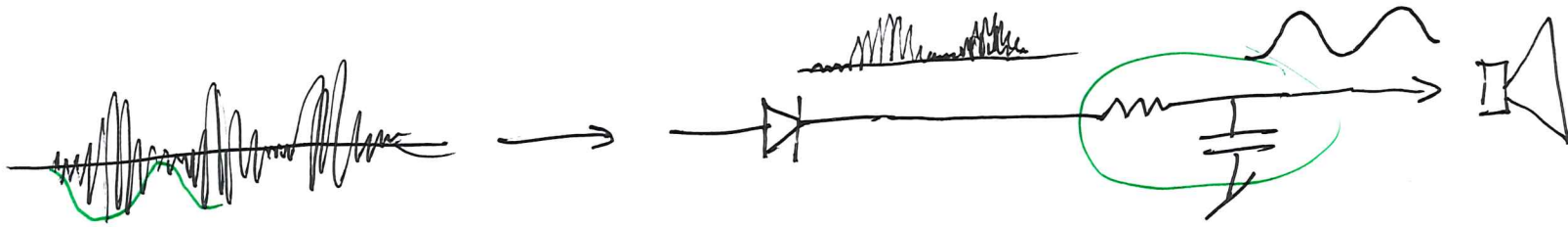

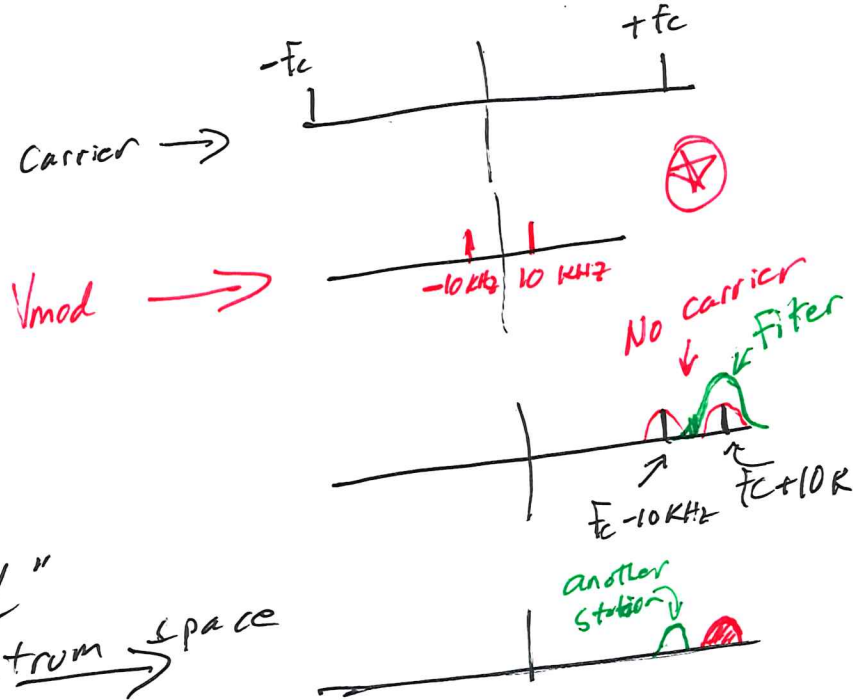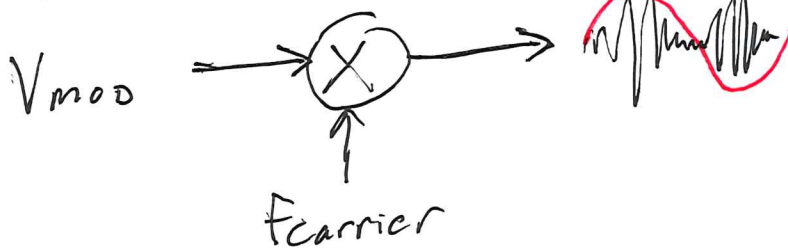More Efficient: "Balanced Modulator"  
 ≡ 4-quadrant multiplier: (negative  $V_{mod}$  reverses phase of carrier)





"Single Side Band"

- minimum use of spectrum  $\rightarrow$  space
- All transmitted power is useful
- balanced modulator and filter at low level  
 - need linear power amplifier after - inefficient
- Demodulation hard - need to supply carrier - Guess Frequency?

# FM

"Frequency Modulation"

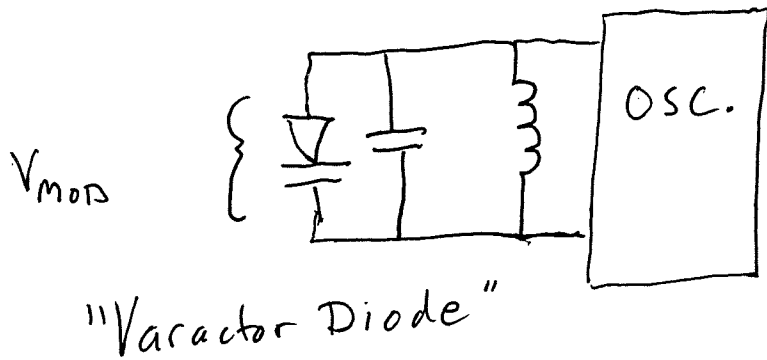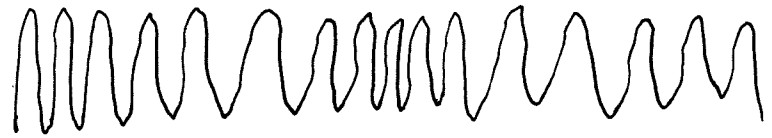

~~FM~~

$f_{max}$  = maximum frequency component of  $V_{mod}$   
(15 kHz for commercial FM)

$\Delta f$  = maximum frequency deviation of carrier produced by  $V_{mod-max}$


"modulation factor"  $h \equiv \frac{\Delta f}{f_{max}}$

$h < 0.5$  "narrow-band FM"

$h \gg 1$  "wide-band FM"


For sine wave at  $F_{max}$ ,  $V_{max}$ .

$h = .1$

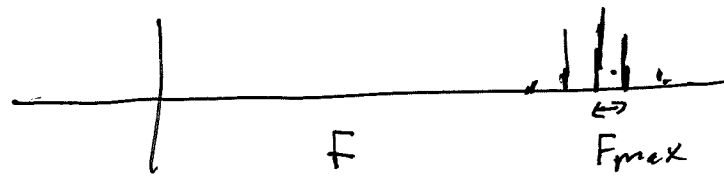

$\sim$  Same as AM

$h = 10$

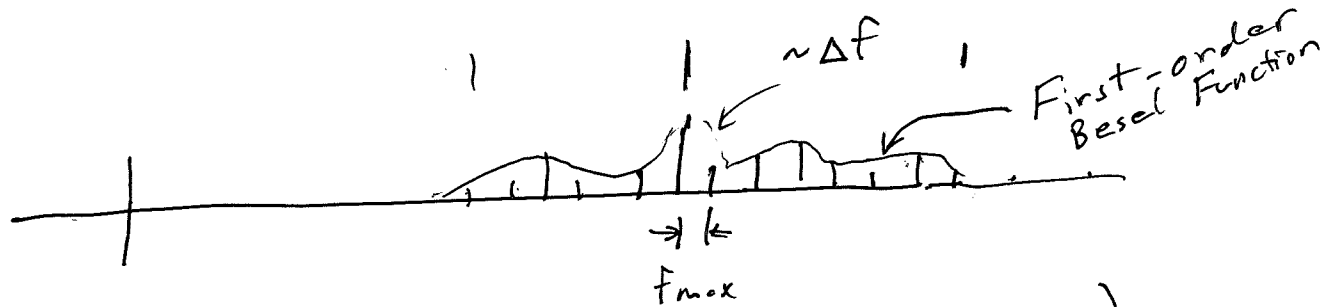


Total Bandwidth (ignoring sidebands  $< 1\%$  of carrier)

$$\approx 2(F_{max} + \Delta f) = 2F_{max}(h+1)$$
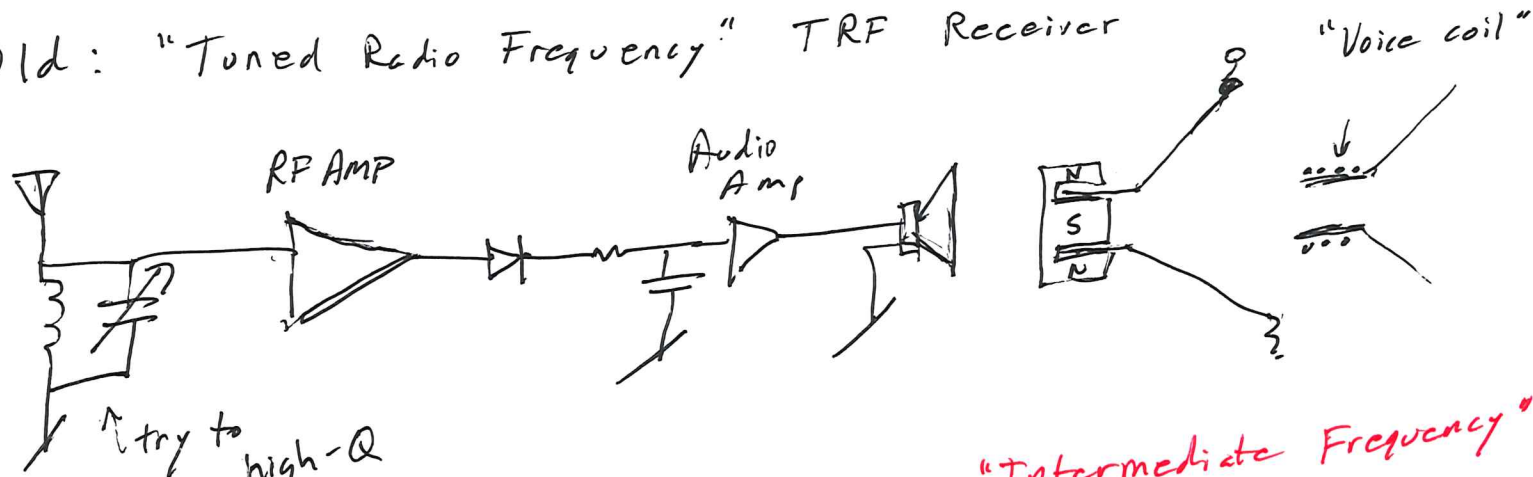
# Heterodyne or "Superheterodyne" Receivers


Old: "Tuned Radio Frequency" TRF Receiver



↑ try to make high-Q to separate stations (but not so high it cuts off modulation)

"Intermediate Frequency"

"Superhet"

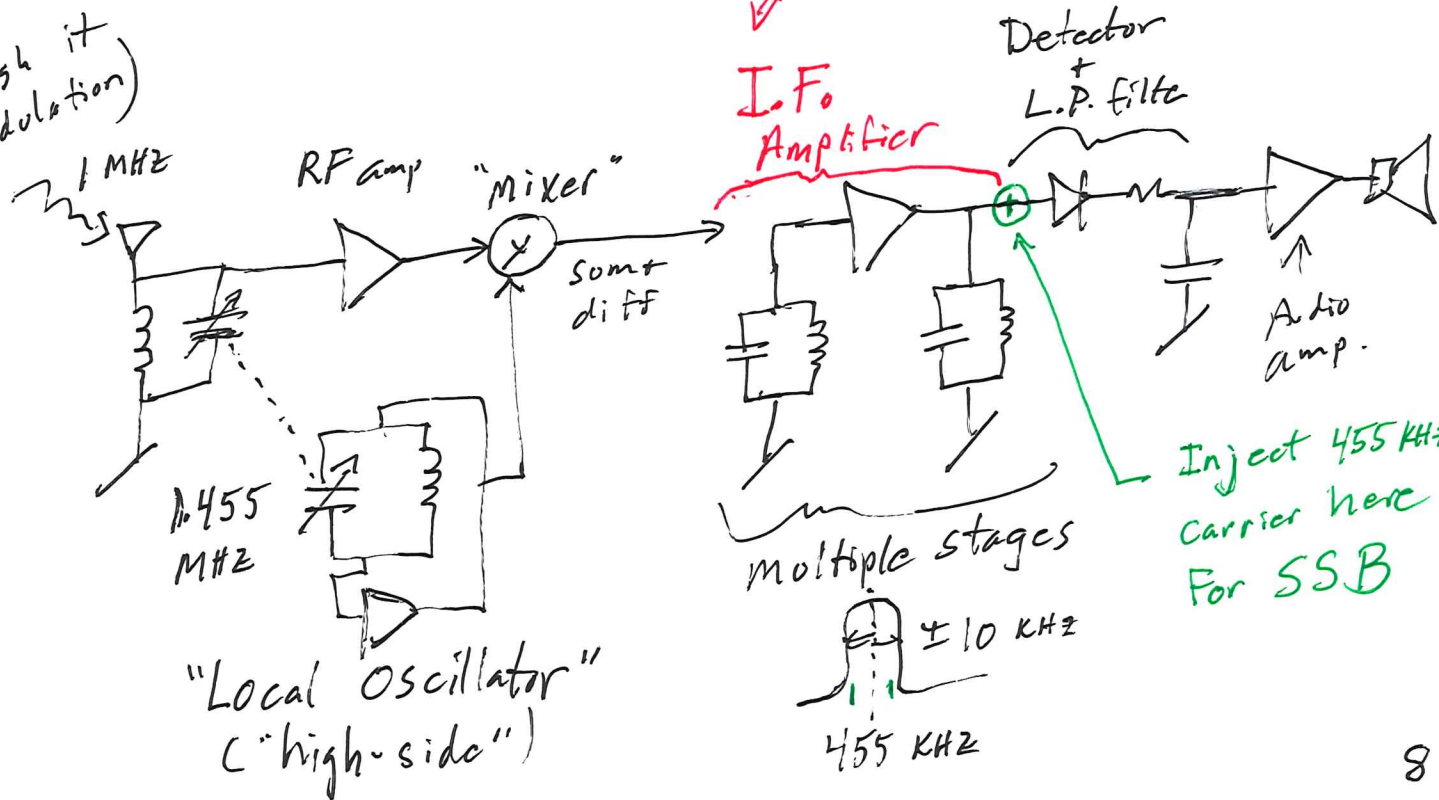


"Local Oscillator" ("high-side")

multiple stages  
± 10 kHz  
455 kHz


Inject 455 kHz carrier here for SSB



# Homodyne Detection

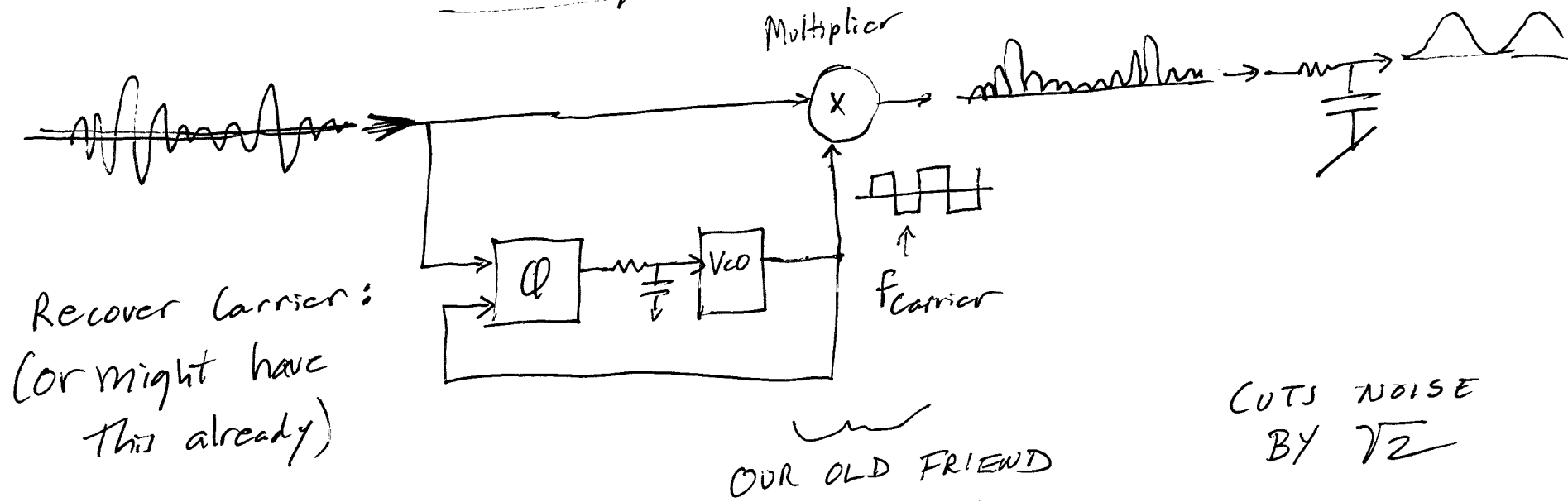



# Bi-Phase Modulation

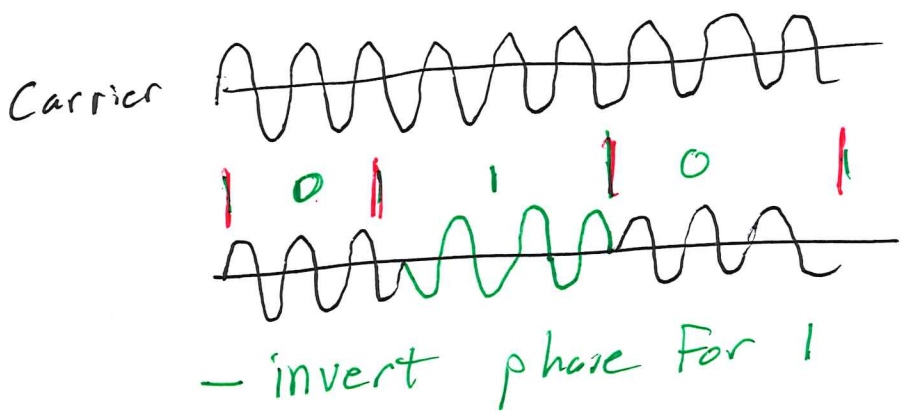

How to demodulate? This is a "balanced modulator"  
- so no carrier. Can't lock a PLL.


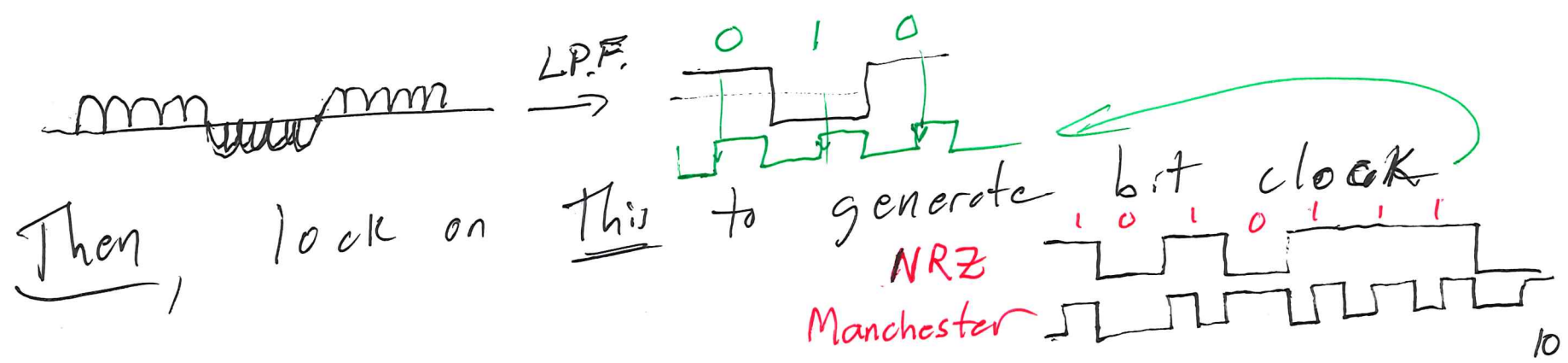
Trick: Square modulated signal: Get continuous sine at  $2F_c$ . Use PLL to lock on this. Divide output by 2.



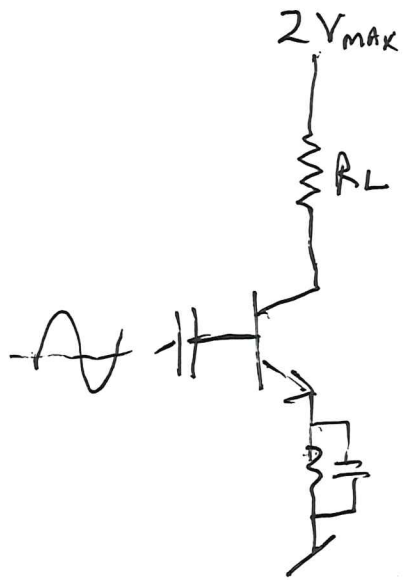

CLASS A  
100% (360°)


$\epsilon \leq 25\%$

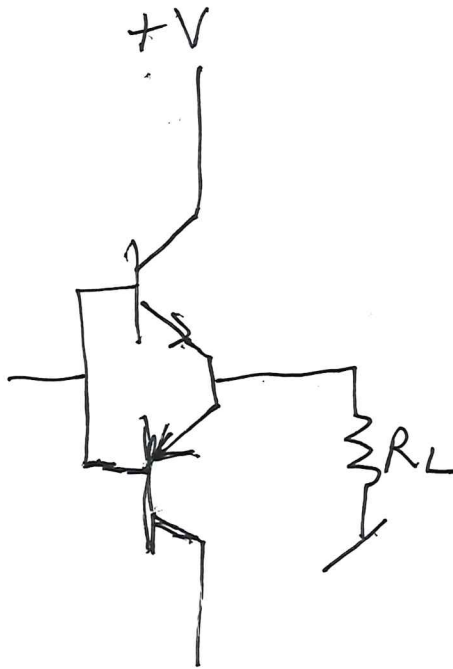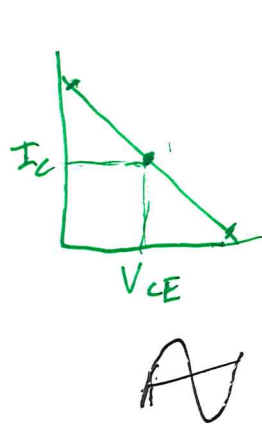

CLASS B  
 $\sim 180^\circ$  (each  $t_p$ )


$\epsilon \leq 50\%$

"Crossover distortion"

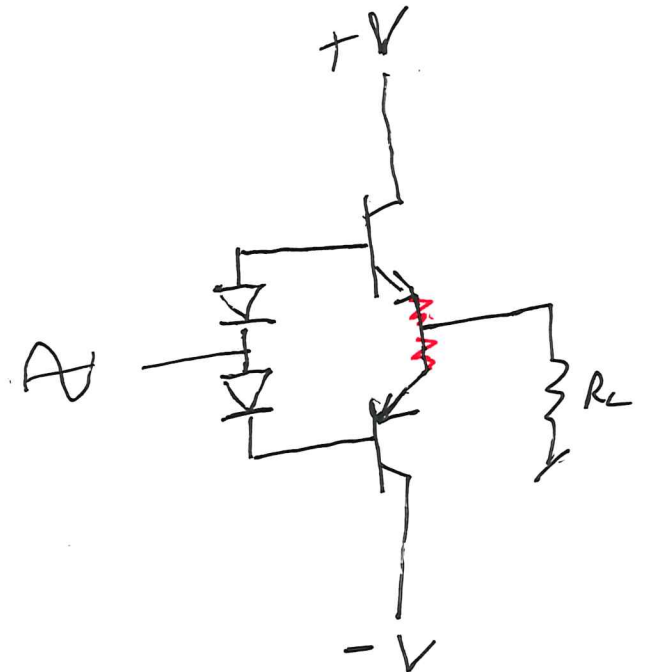

CLASS AB  
 $> 180^\circ$



Stability?  
vs  
Efficiency

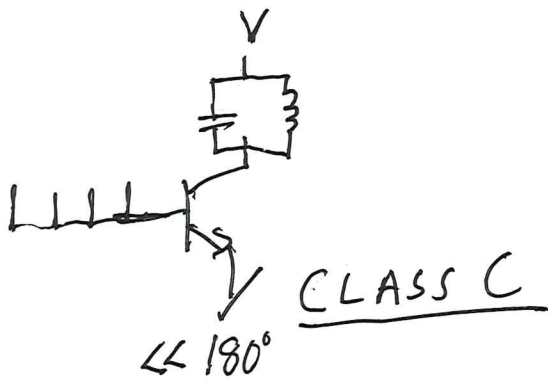

CLASS C  
 $\ll 180^\circ$

$\epsilon < 100\%$

CLASS D  
"Pulse-width Modulation" (PWM)

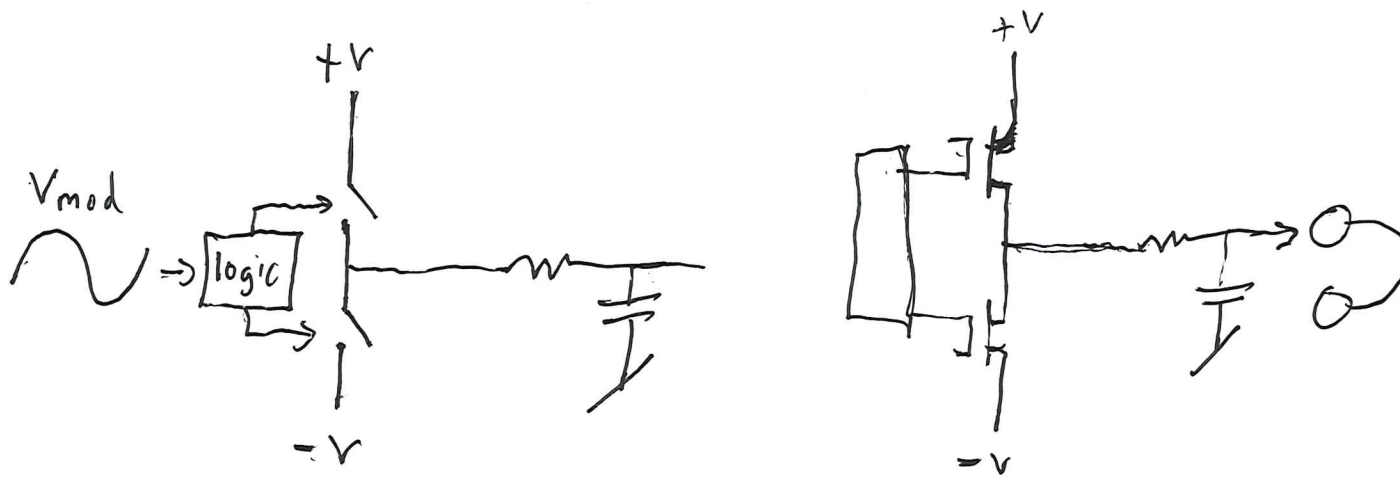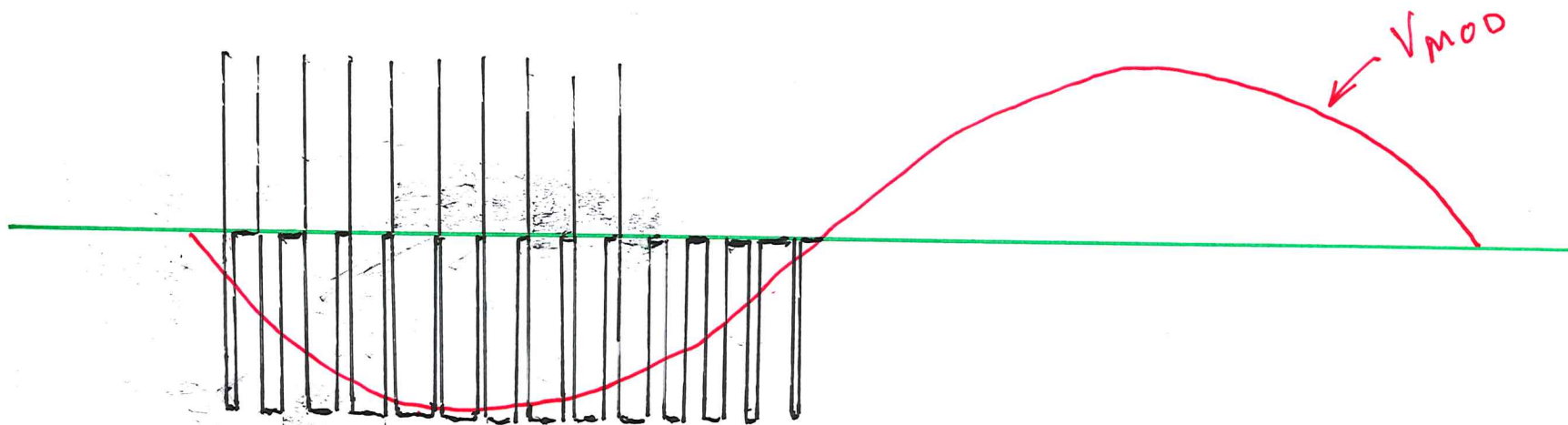


# Digital Signals

Win by going to modest SNR (3 db is plenty). Noise will introduce some errors, but use error correcting codes embedded in bit stream, to detect and correct errors.

0 1 0 1 0 0 1 0

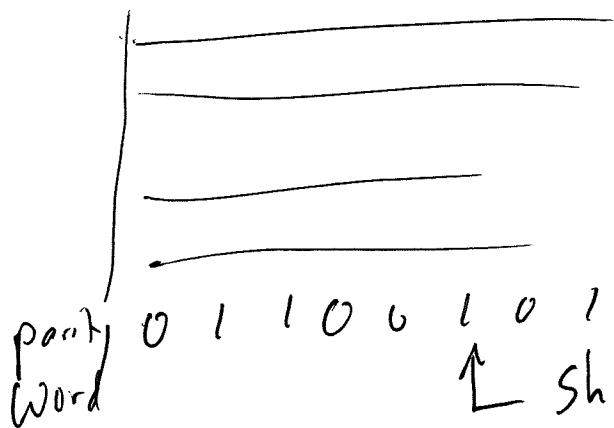↓ parity bit ensures odd # of 1's if correct



↑ should have odd # in column