

Ph 623 - March 31<sup>st</sup>

- Digital Prelab due tomorrow
- Exam II next Tuesday
- HW 9 due ~~next~~ Thursday, April 9
  - Available on course website
  - Good practice for exam, however!

To day:



Phase-locked Loops

(Real 13.13)

Problems they can solve:









1. How do you identify the tones the telephone pushbuttons make?
2. How do you generate a 2 GHz clock for your computer from a 10 MHz crystal reference?
3. How do you know when to look at the bits in a digital data stream from a satellite? ("Clock regeneration")
4. How do you make a digital "frequency synthesizer" where you put in a number and get an output at that many Hz? (It needs to be referenced to a crystal oscillator or atomic clock frequency standard.) - There's one in every radio receiver these days.
5. How do you lock a laser to a fixed difference from another laser?

Phase-locked loop is a feedback loop.

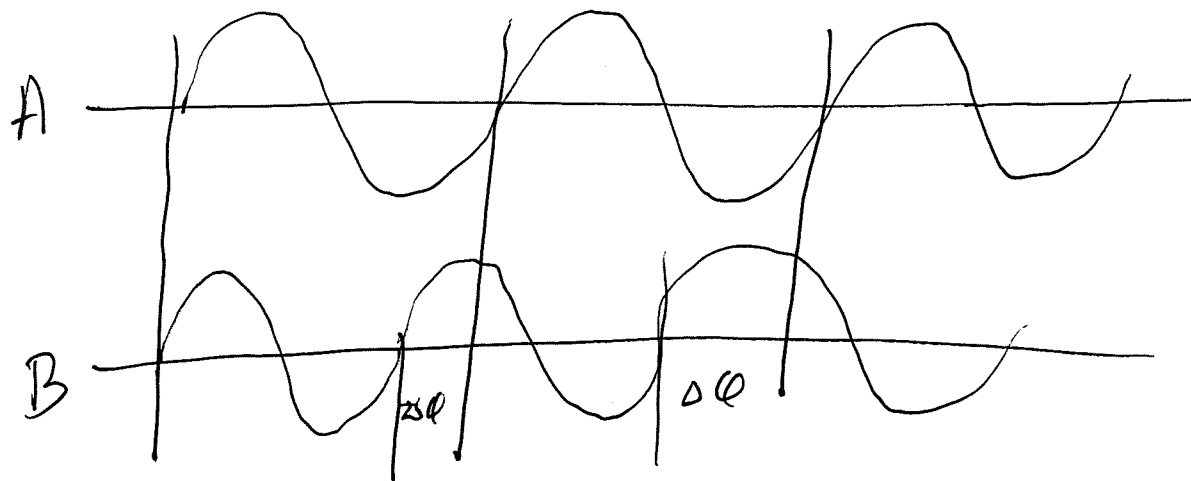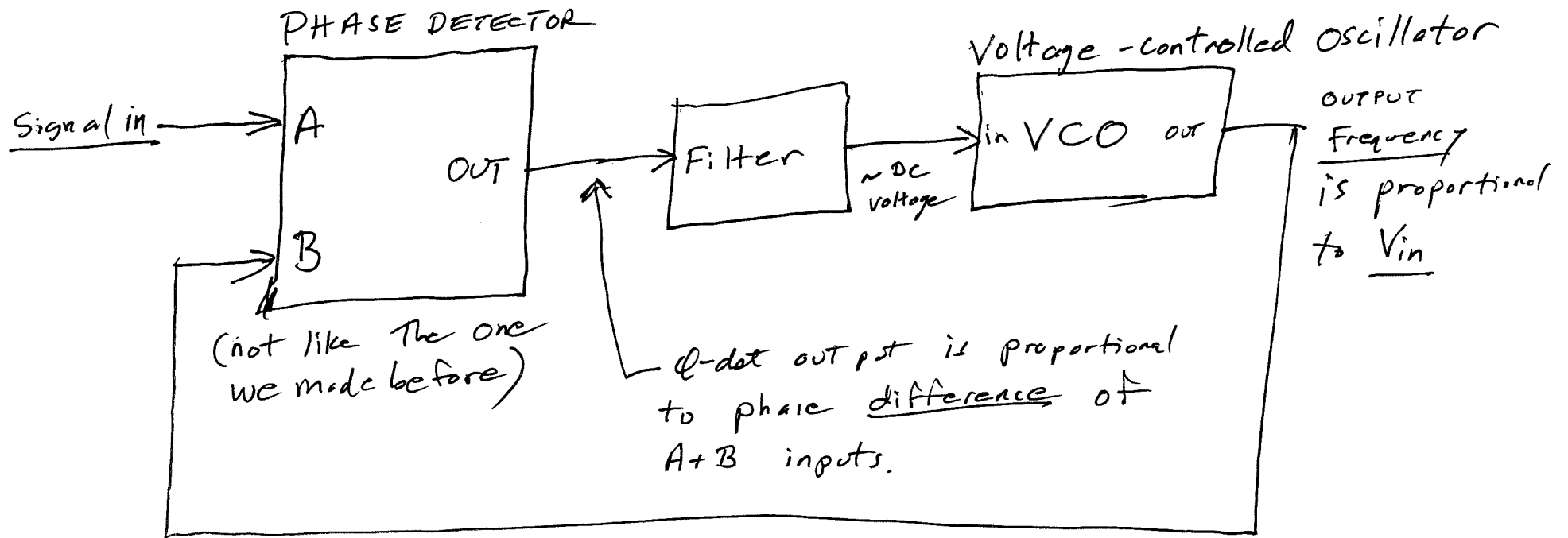


Phase difference  $\Delta\phi$  is integral of Frequency difference


# Type I Phase Detector

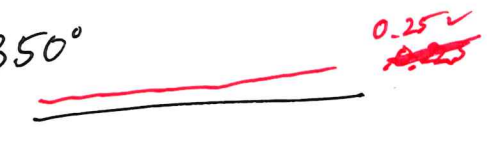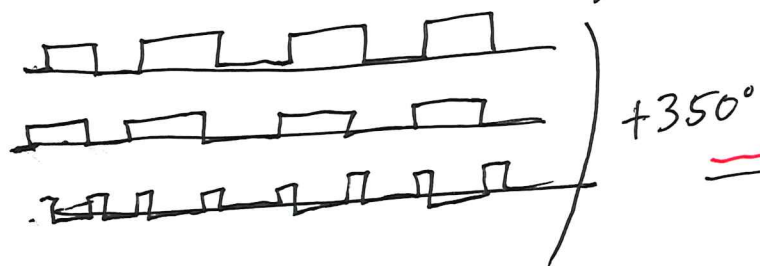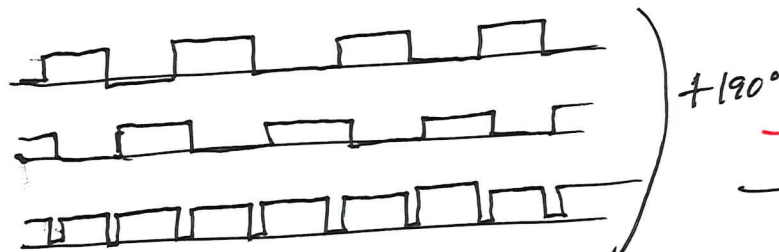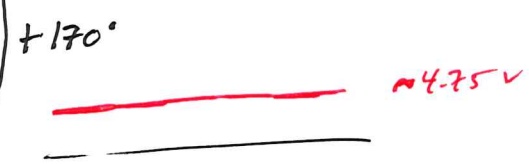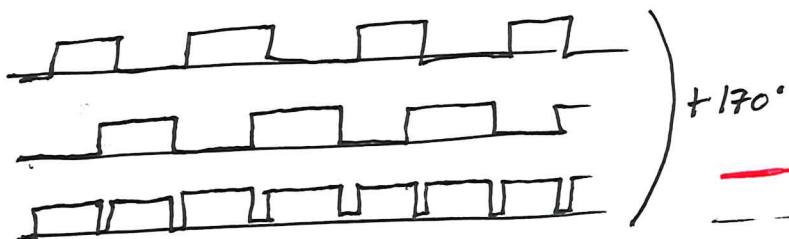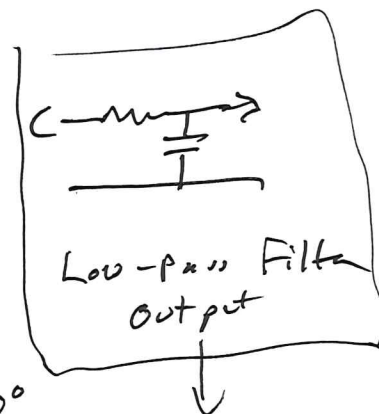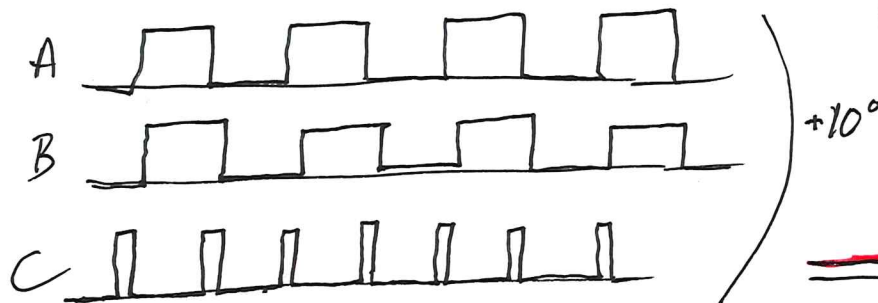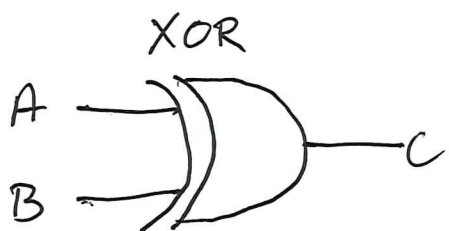


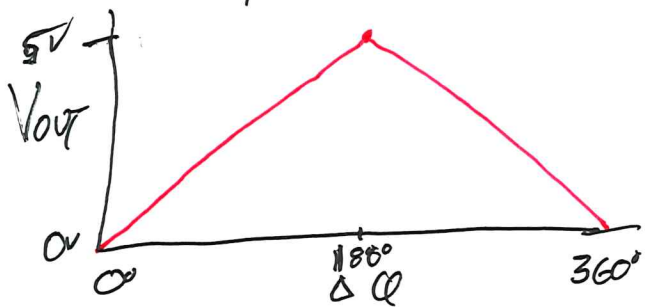
## Transfer Function

$\Delta \phi \rightarrow V_{out} \text{ from Filter}$



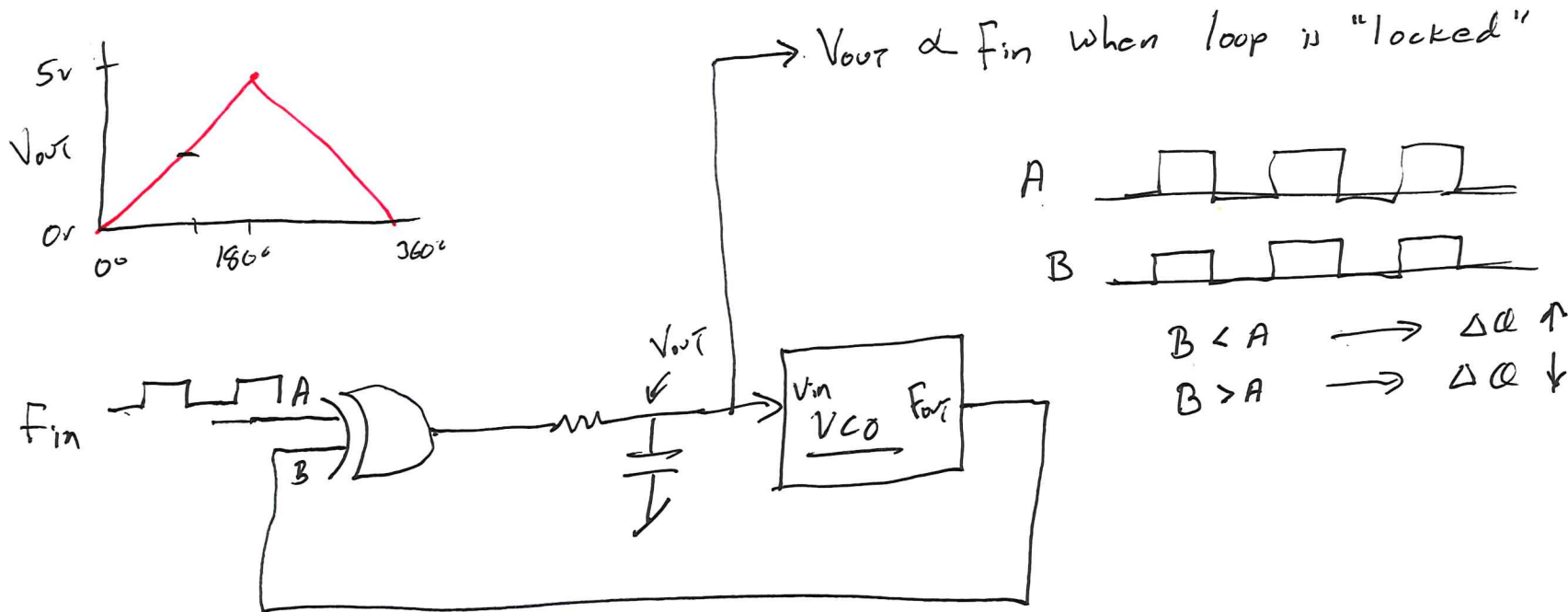

VCO Transfer Function

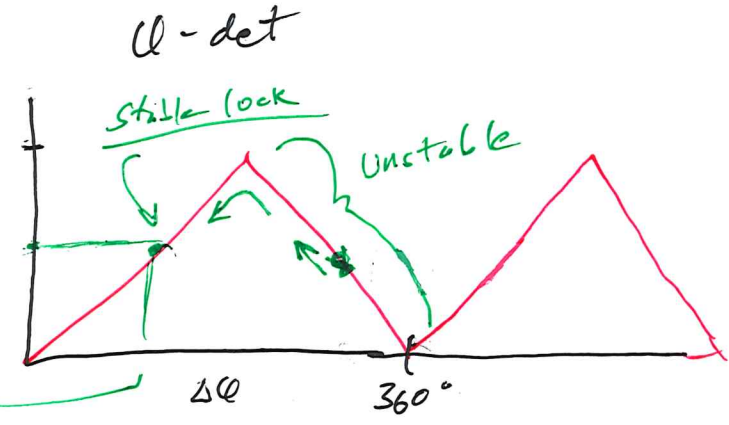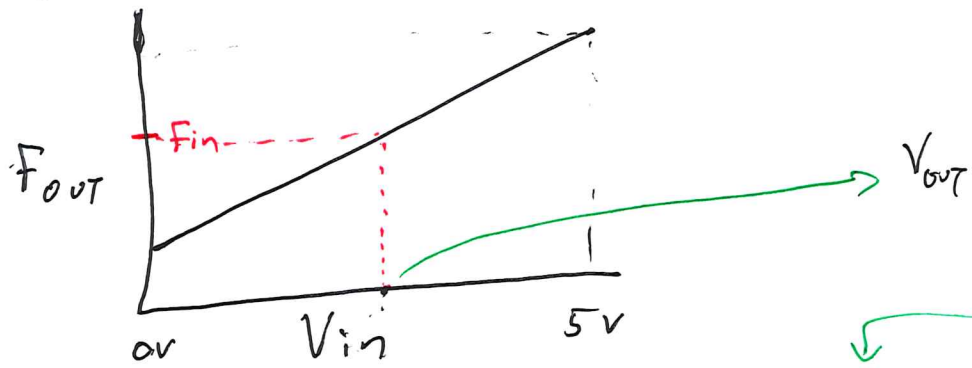

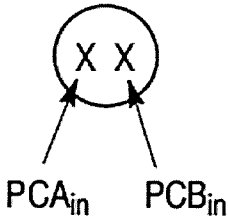
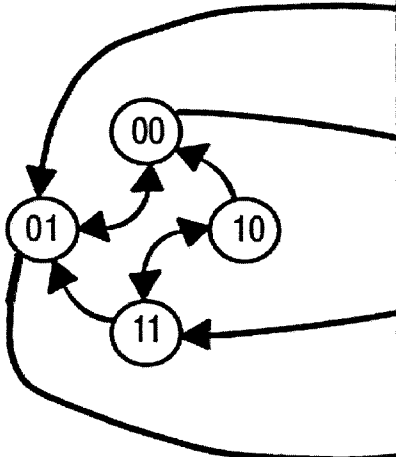
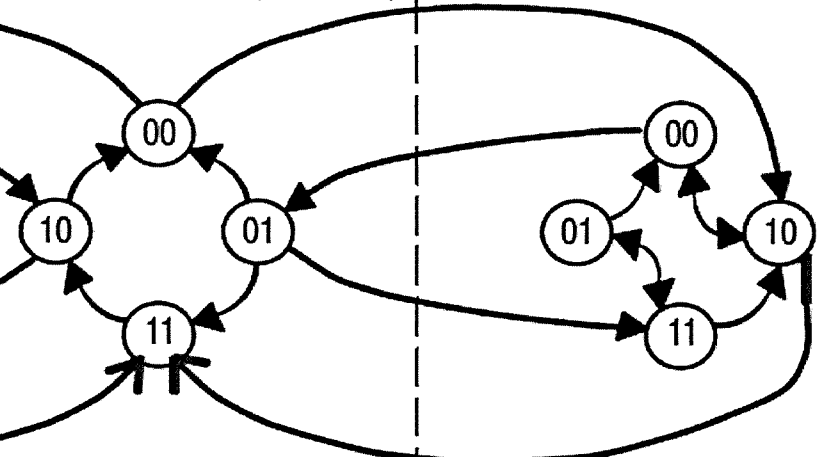
↑ will stop at  $\sim 90^\circ \Delta\phi \rightarrow 2.5v$

Type I

- Stabilizes ("Locks") with a  $\Delta\phi = 0^\circ \rightarrow 180^\circ$
- Requires square wave input on A and B.


# Type II

## PHASE COMPARATOR 2 (Edge-triggered)

	<b>PHASE COMPARATOR 2 (Edge-triggered)</b>		
<p>Input Stage</p> 	<p>(A<sup>^</sup> --&gt;)</p> 	<p>(A<sup>^</sup> --&gt;)</p> 	
	<p>(&lt;--B<sup>^</sup>)</p>	<p>(&lt;--B<sup>^</sup>)</p>	
PC2 <sub>out</sub>	0	3-State Output Disconnected	1
LD (Lock Detect)	0	1	0



# Type II Q-det

Consoll MC14046B Data sheet From website

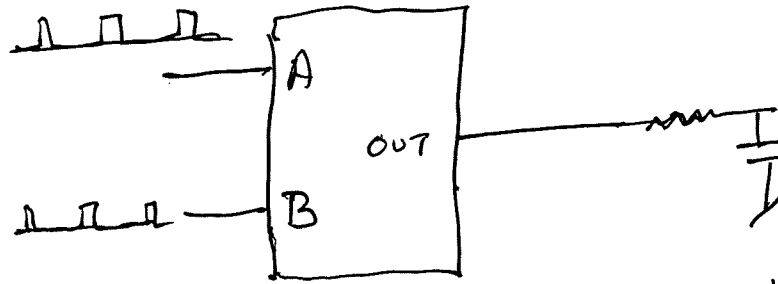

Easiest to think of as


State Machine

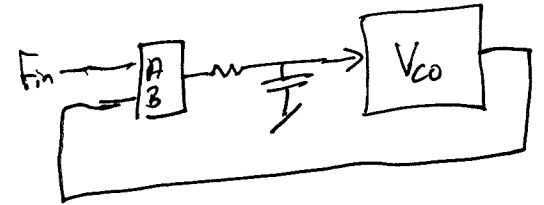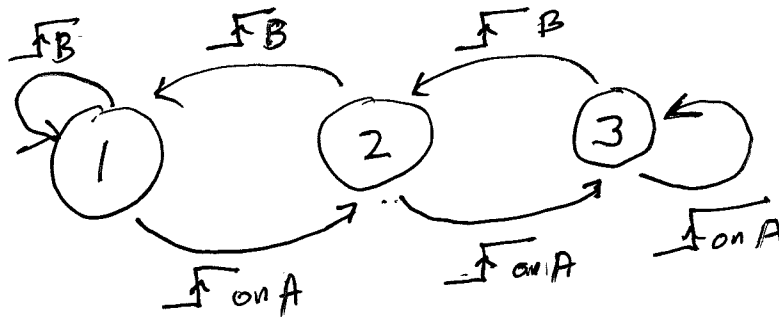


①  
⇒ OUTPUT IS LOW

②  
⇒ OUTPUT High Impedance (open circuit)

③  
⇒ OUTPUT is HIGH

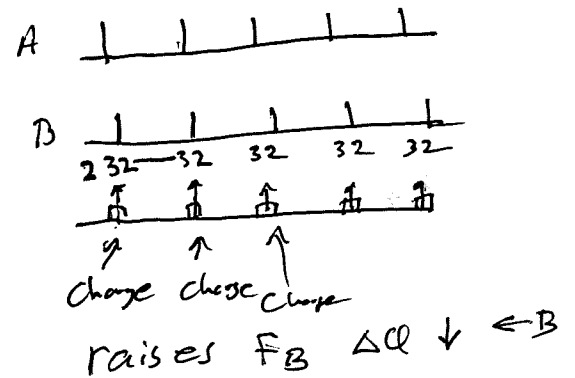


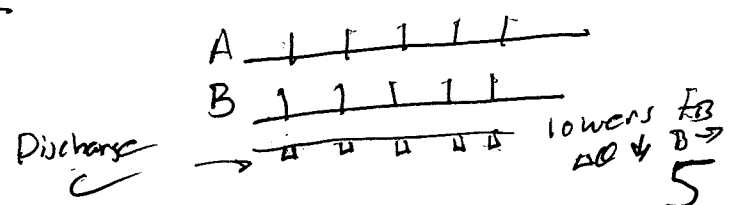1. Always Locks with  $\Delta Q = 0^\circ$
2. Duty cycle doesn't matter → only sees (more sensitive to noise on Fin)



COULD also make type II with current


Sources :

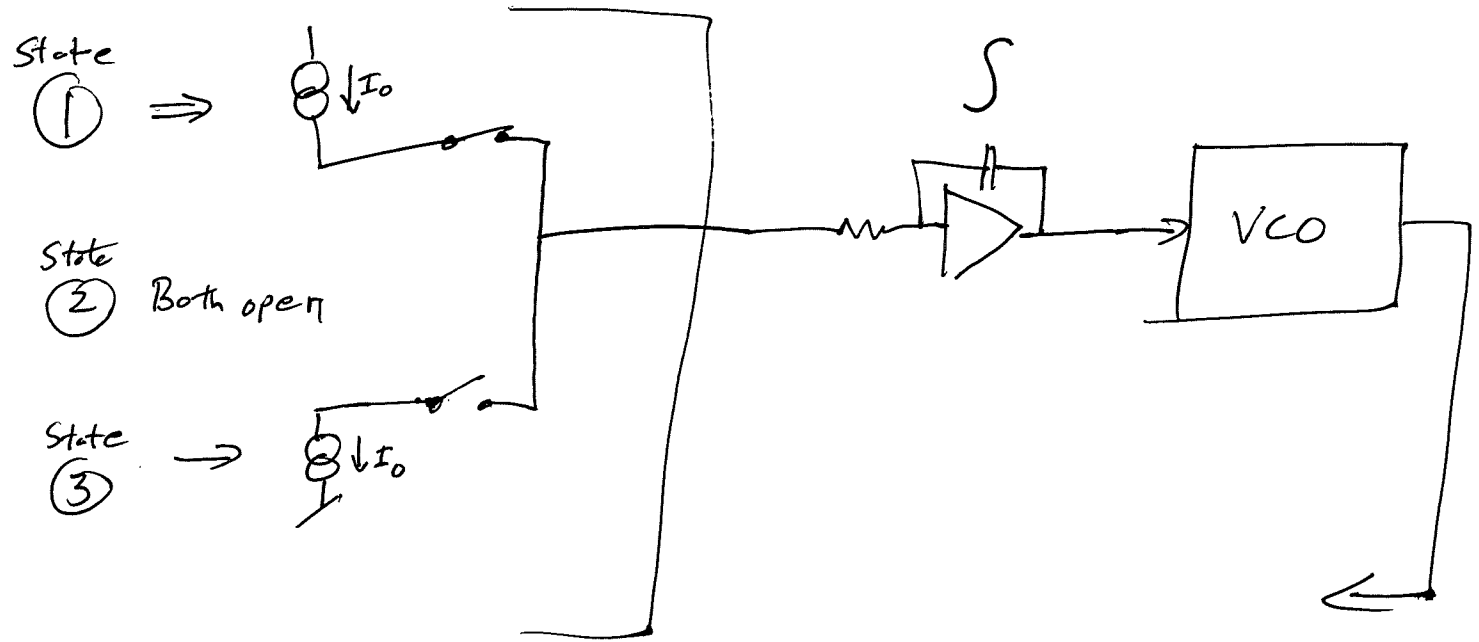

Type I can also use an analog multiplier.



This is like our old phase detector, where the signal is input A + phase reference is input B. When  $F_A \equiv F_B$ , after low-pass filter (to remove  $A+B$ ) Get  $(A-B) = \text{Zero F or D.C.} * \cos(\Delta\phi)$

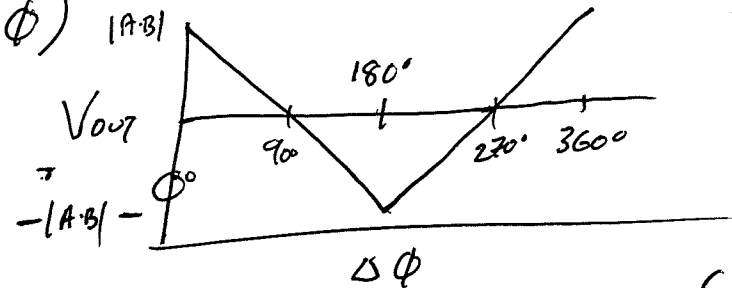IF it is very linear + B has amplitude  $\equiv 1.000$ , then this is same as our lock-in circuit.




# "Capture"

Easy with type II:

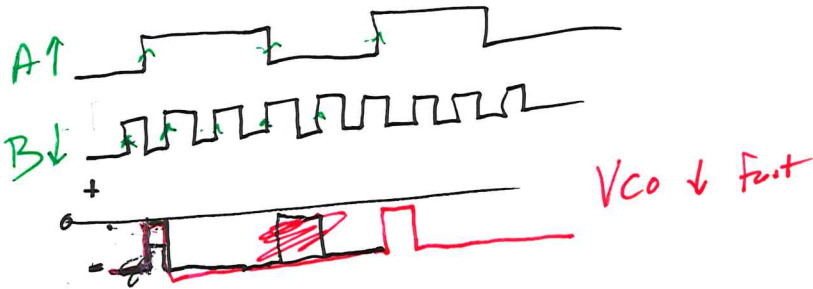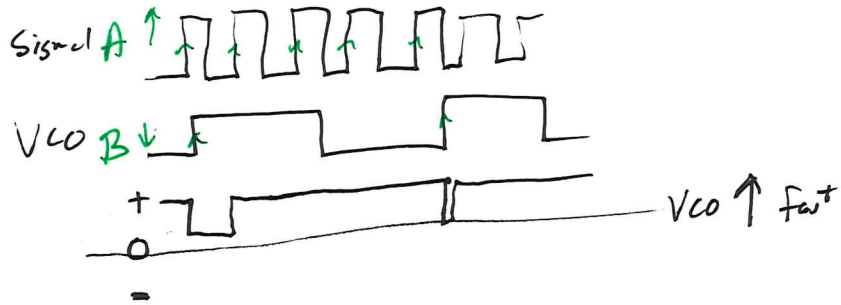

Pretty wild with Type I:

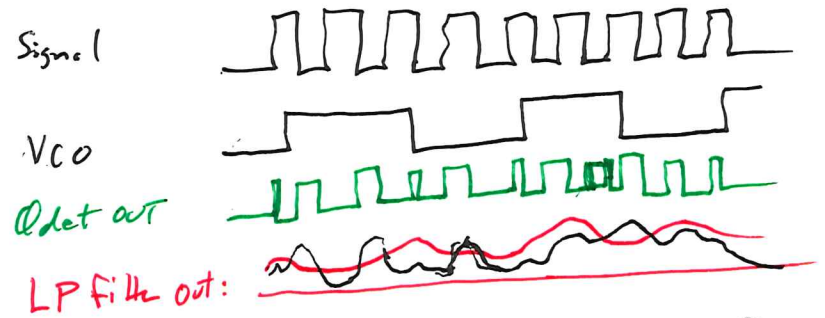

Capture is complicated function of filter response.

"Capture range"  $\equiv$  range of signal frequencies where initially unlocked signal will be locked to.





"lock range"  $\equiv$  range of signal frequencies where VCO will follow once it is locked.

- Type I: Capture range: Depends on filter; lock range = range of VCO
- Type II: Capture range = lock range = range of VCO



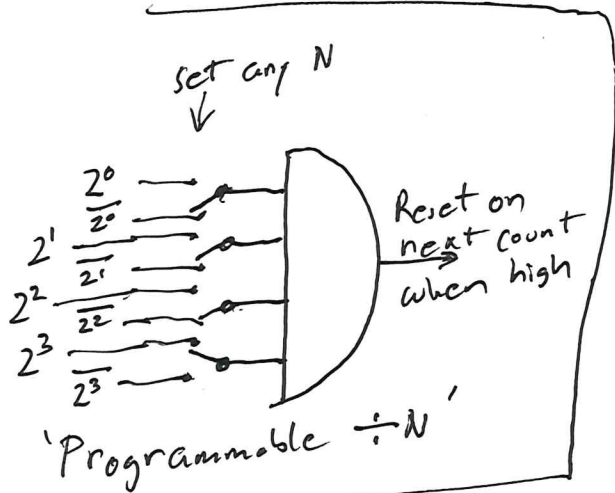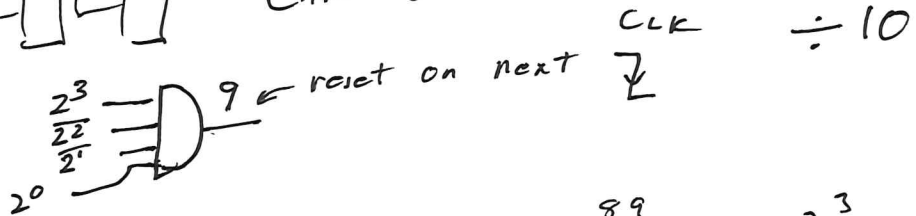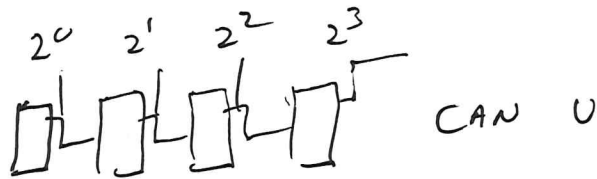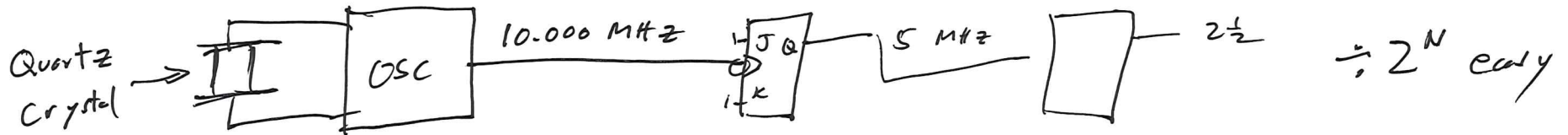
# Applications

Frequency Multiplier? Easy to make divider:



CAN MAKE  $\div N$

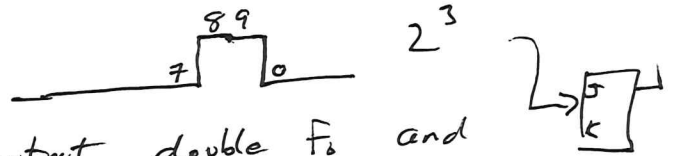
If we need a square output, double  $f_i$  and add one more toggle




But how to get 2 GHz from 10 MHz?

Remember Op-amp circuits? Putting a function in a negative feedback loop  $\rightarrow$  inverse function.



### Frequency Multiplier

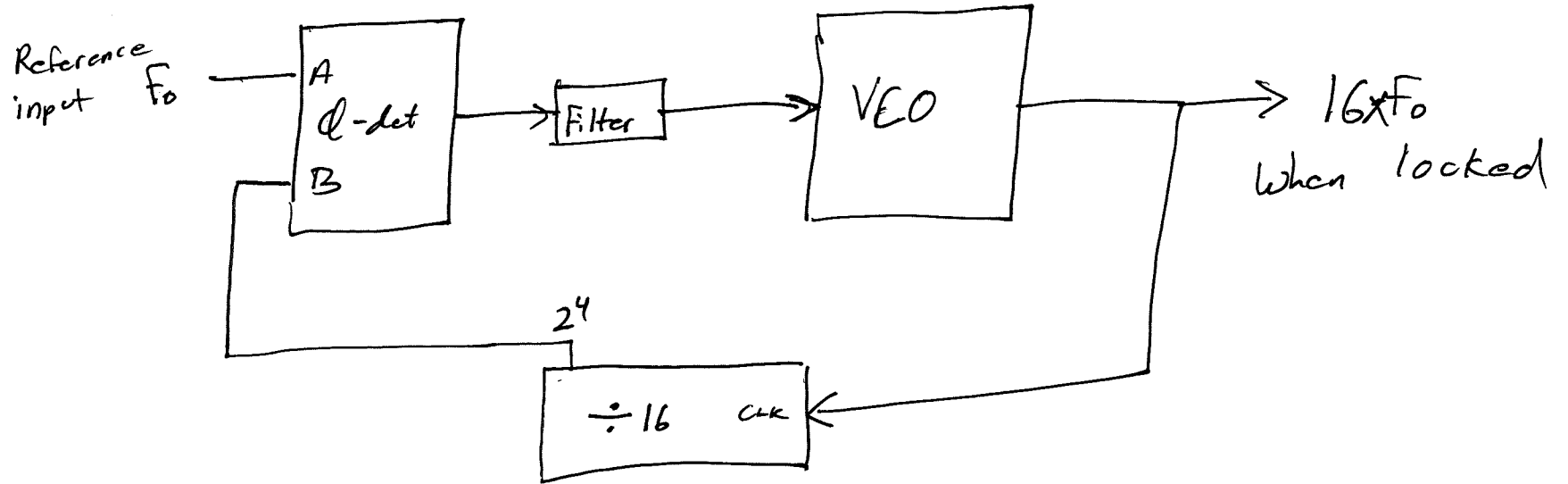


### Frequency Synthesizer

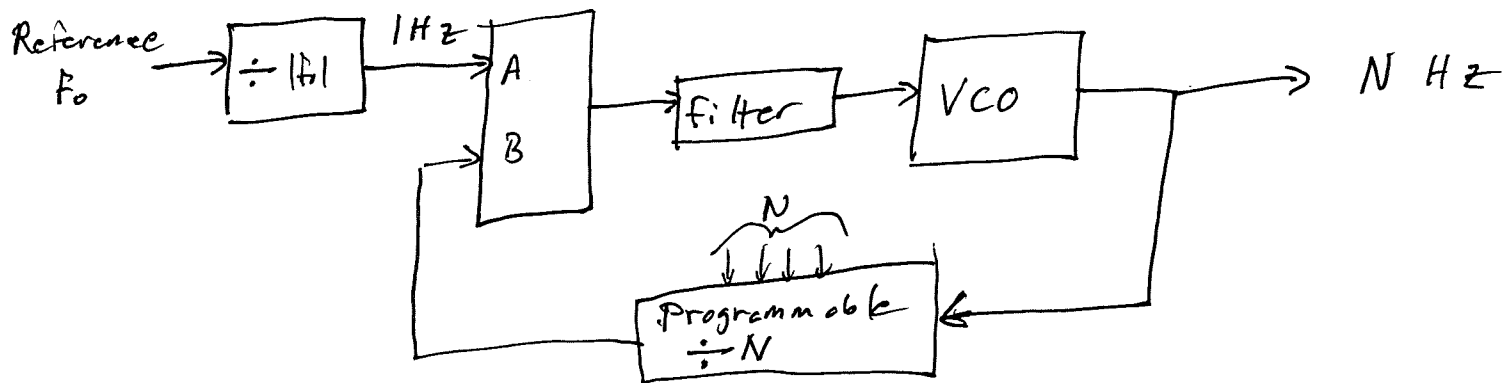

# FM demodulation

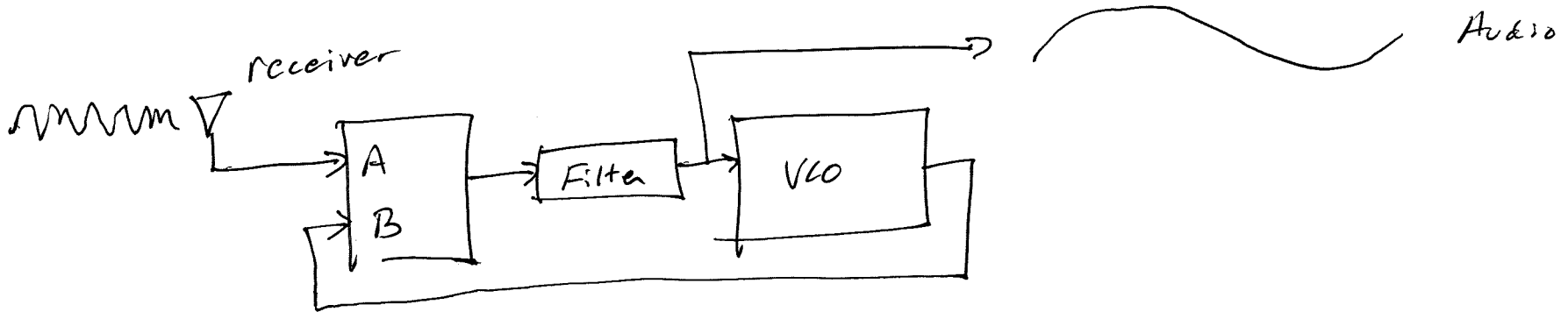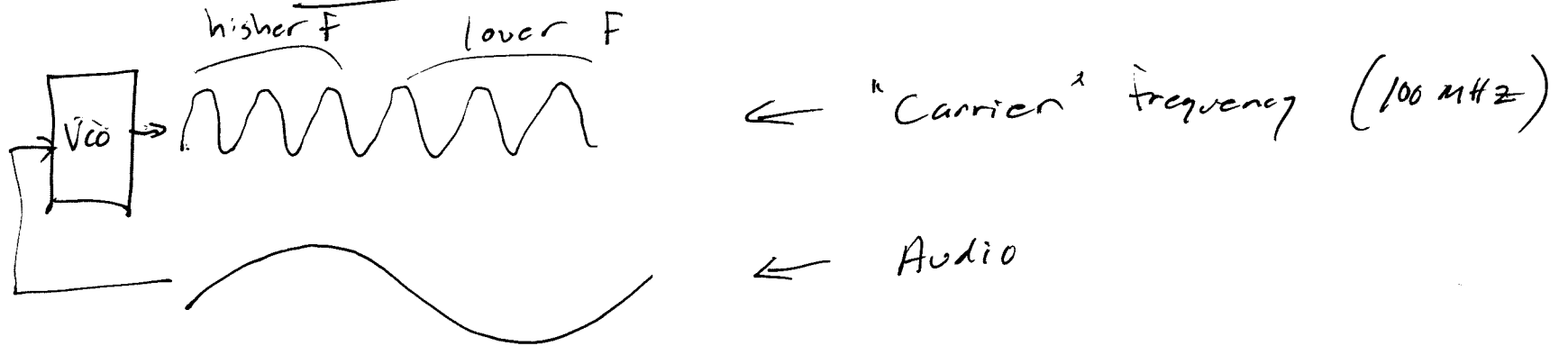


# Laser offset lock

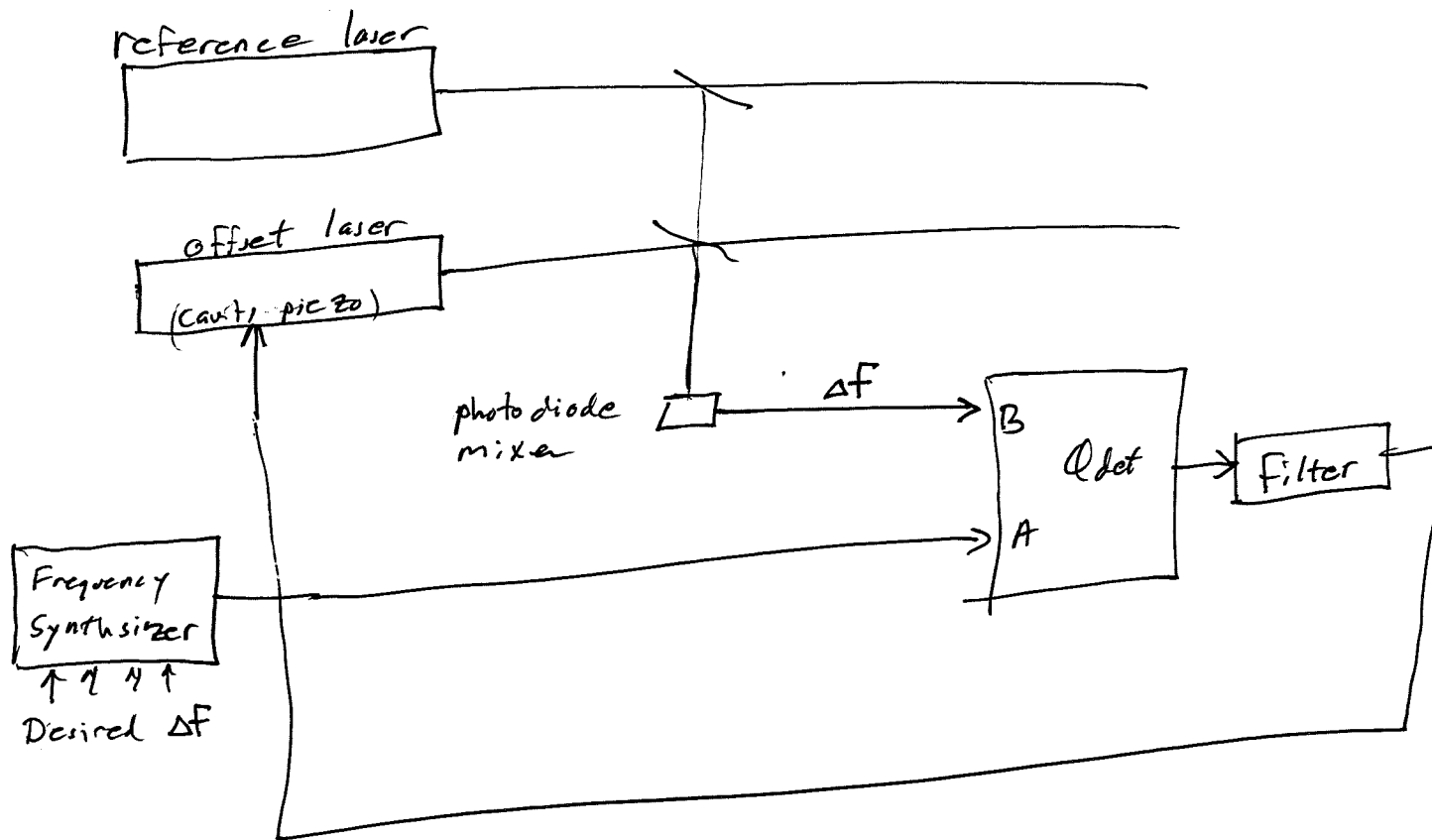


# VCOs


low frequency

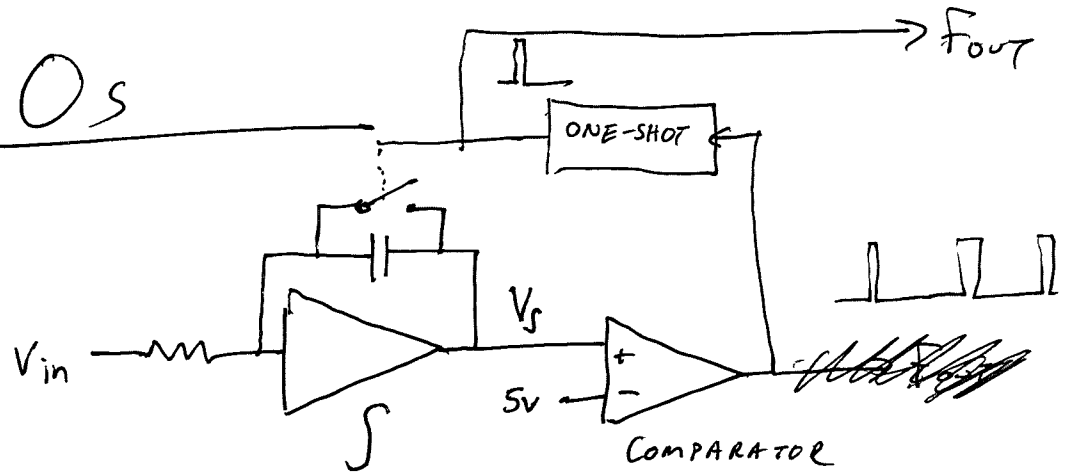

very linear

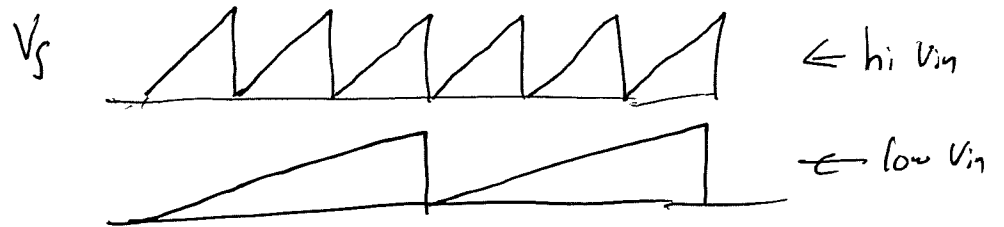

high frequency

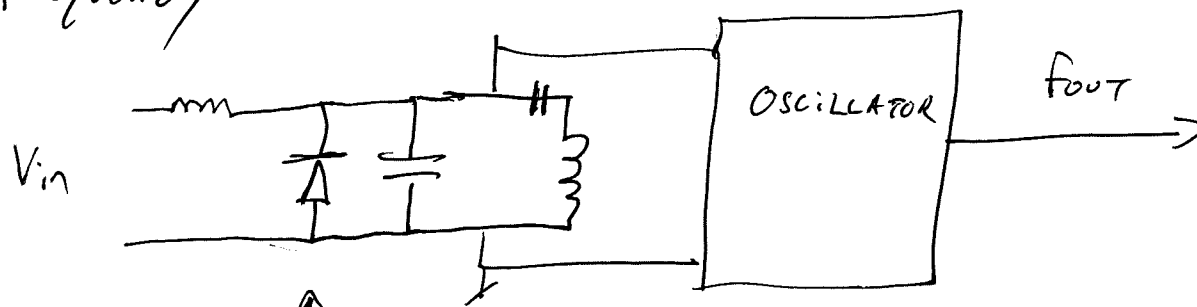

"Varactor Diode"  
reverse bias,  $C$  depends on  $V_{reverse}$

not so linear