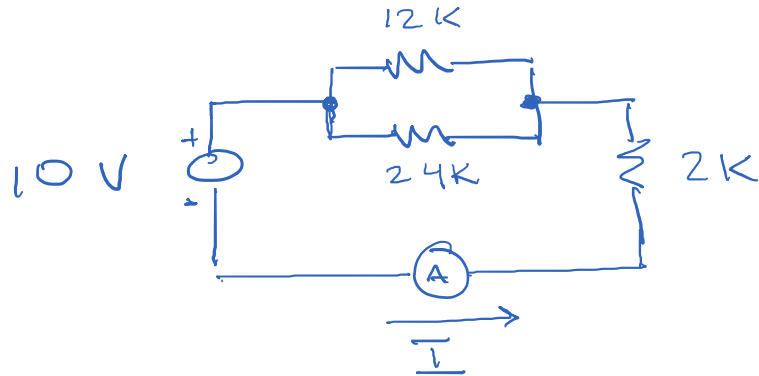


# PHYS. 623 PS #1

1.




FIND CURRENT  $I$

NOTE:  $2K = 2000 \Omega$ , ETC.

— (A) — IS AMMETER  
[ POSITIVE CURRENT DEFINED  
IN DIRECTION OF ARROW ]

2.

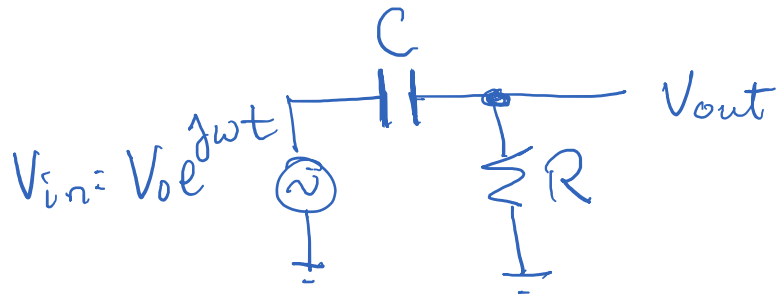


A.  $\left| \frac{V_{out}}{V_{in}} \right| = \underline{\hspace{2cm}}$

SOLVE AS  
FUNCTIONS  
OF  $\omega$


B.  $\phi \left( \frac{V_{out}}{V_{in}} \right) = \underline{\hspace{2cm}}$

3. A. SKETCH  $\left| \frac{V_{out}}{V_{in}} \right|$  vs.  $\omega$  ON LOG-LOG PLOT FOR #2.

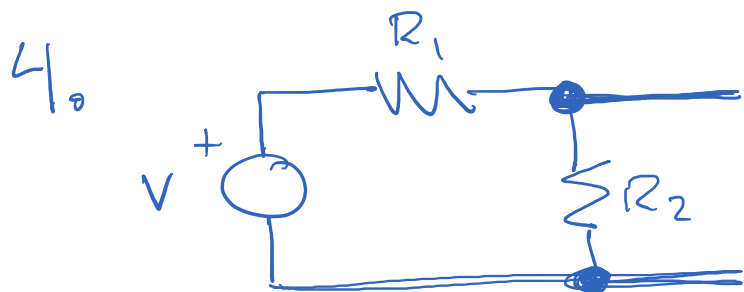B. SKETCH  $\phi$  vs.  $\omega$  ON SEMILOG PLOT FOR #2.  
(LOG IN  $\omega$ )



FIND THEVENIN EQUIVALENT

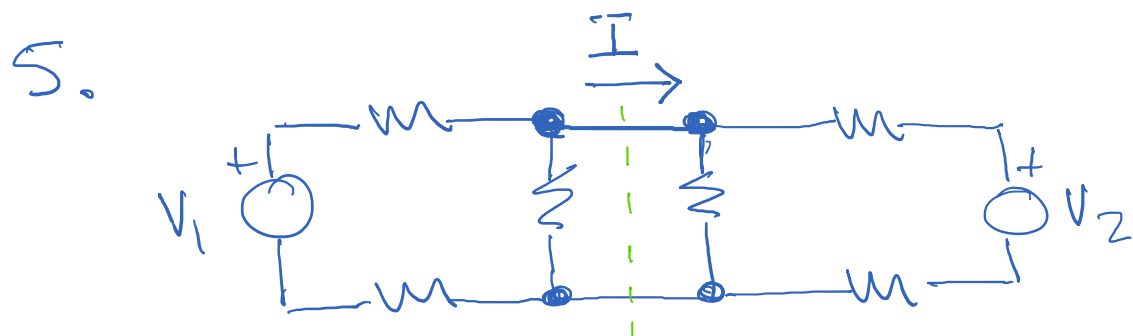

ALL RESISTORS HAVE VALUE  $R$

FIND  $I$  IN TERMS OF  $V_1, V_2$  &  $R$ .

HINT: FIND THEVENIN EQUIVALENTS OF LEFT & RIGHT HALVES, THEN CONNECT THEM TOGETHER


6.

CONSIDER A SOURCE WITH OUTPUT RESISTANCE  $R$ . FOR WHAT VALUE OF LOAD RESISTANCE  $R_L$  IS POWER TRANSFERRED TO LOAD MAXIMUM? WHAT IS MAX. POWER DELIVERED TO THE LOAD? SEE DIAGRAM.


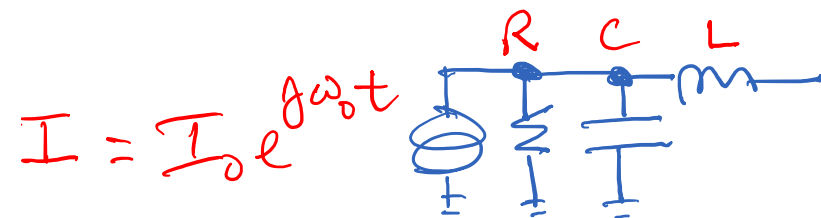
## 7. RESONANT IMPEDANCE TRANSFORMER

CONSIDER THE CIRCUIT BELOW; HERE  $\omega_0 \equiv \frac{1}{\sqrt{LC}}$ .



EXPRESS AS A NORTON EQUIVALENT. WORK IN LIMIT  $Q \equiv \frac{R}{\omega_0 L} = \omega_0 RC \gg 1$ .  
WRITE YOUR ANSWER IN TERMS OF  $I$ ,  $R$ , AND  $Q$ .