
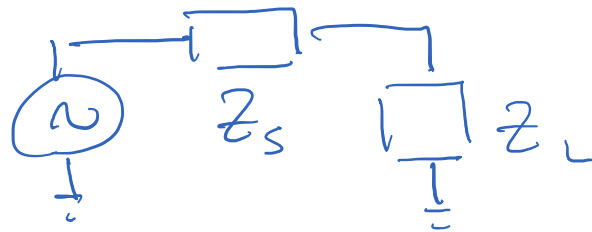


Problem Set 2

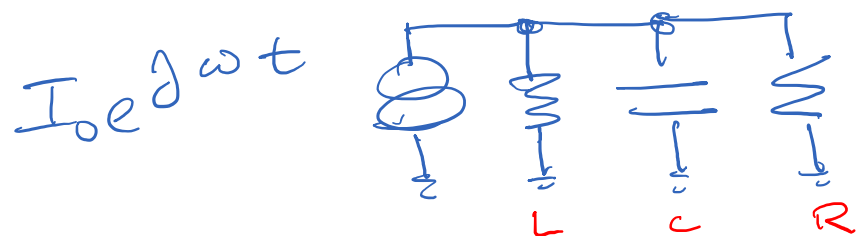1. Consider a source with complex output impedance Z_S . Find load impedance Z_L that provides maximum power transfer from source to load.



2. LCR TANK CIRCUIT



introduce

$$\omega_0 \equiv \frac{1}{\sqrt{LC}}$$

$$Z_0 = \omega_0 L = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}}$$

$$Q = \frac{R}{Z_0} \gg 1$$

$$\Delta \equiv \omega - \omega_0$$


A. FIND $V_R(\Delta)$

B. FIND $I_L(\Delta=0)$

C. FIND $I_C(\Delta=0)$

EXPRESS ALL ANSWERS IN TERMS OF I_0, Z_0, Q, Δ .

3. Horowitz & Hill EXERCISE 1.44

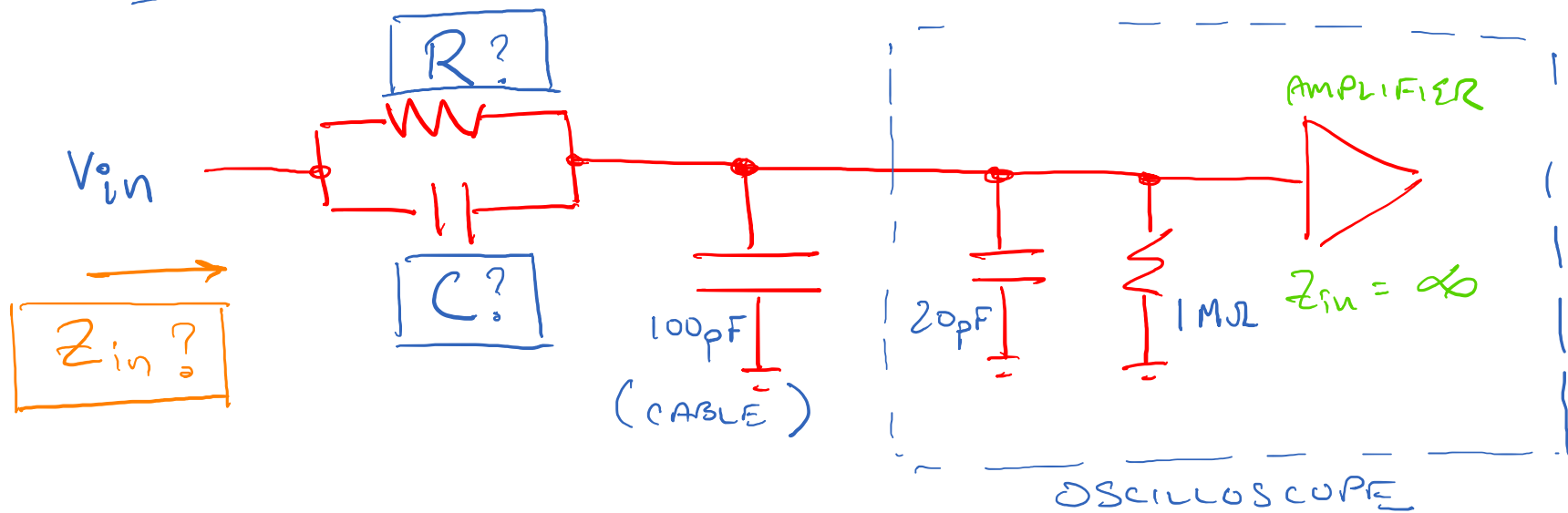

A.

FIND R & C SO THAT SIGNAL DELIVERED TO AMP INPUT IS $V_{in}/10$ @ ALL FREQUENCIES.

B. WHAT IS COMPLEX INPUT IMPEDANCE Z_{in} ?

[CAN EXPRESS AS A RESISTANCE IN PARALLEL w/ A CAPACITANCE]